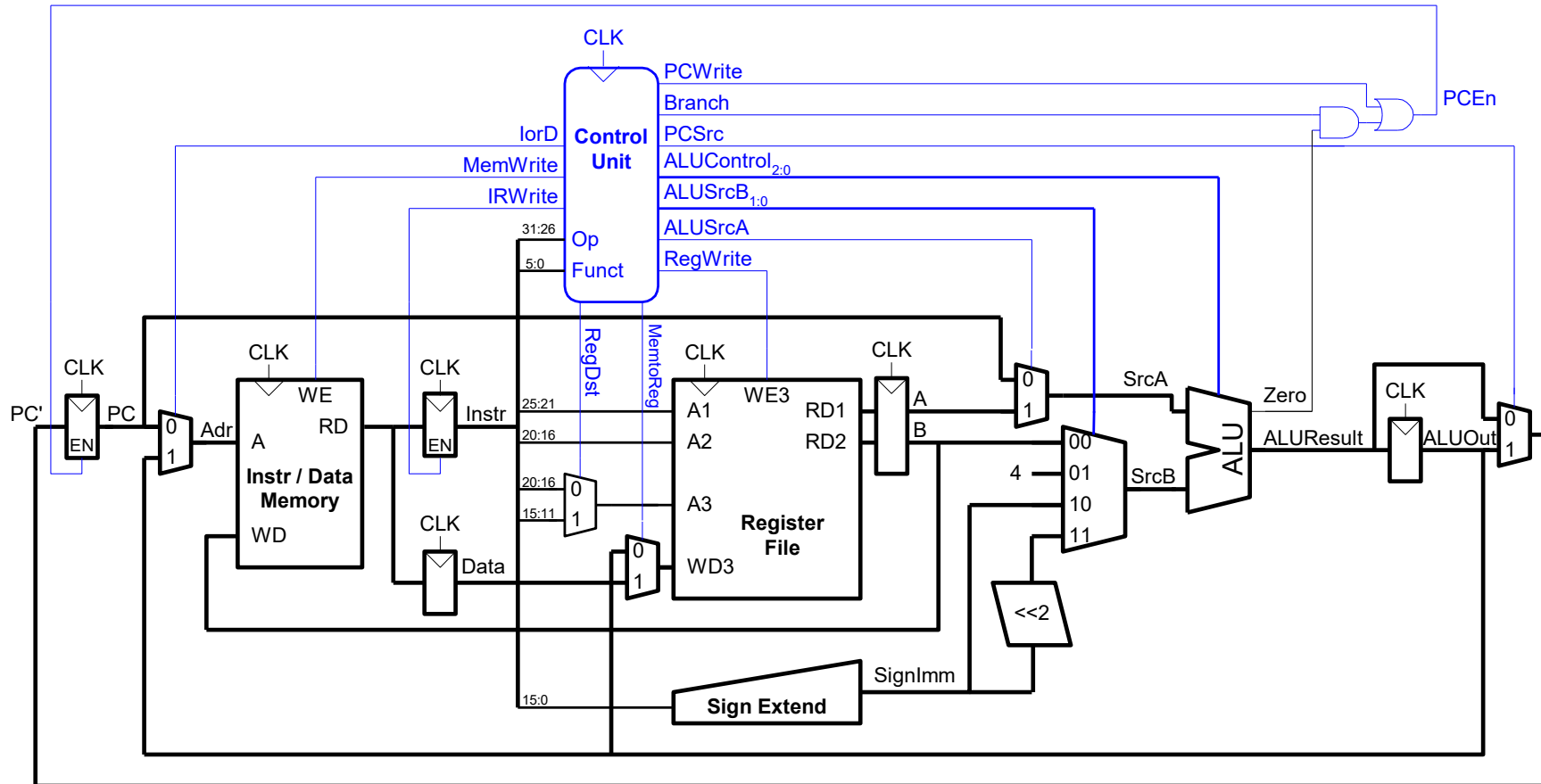



MIPS microarchitecture

These transparencies are based on those provided with the following book:
David Money Harris and Sarah L. Harris, “Digital Design and Computer Architecture”,
2nd Edition, 2012, Elsevier

Multicycle Processor Architecture




Multicycle Processor Architecture

 

The processor is organized in 2 parts:


- Data Path (in black)
- Control Unit (in blue)

Multicycle Processor Architecture

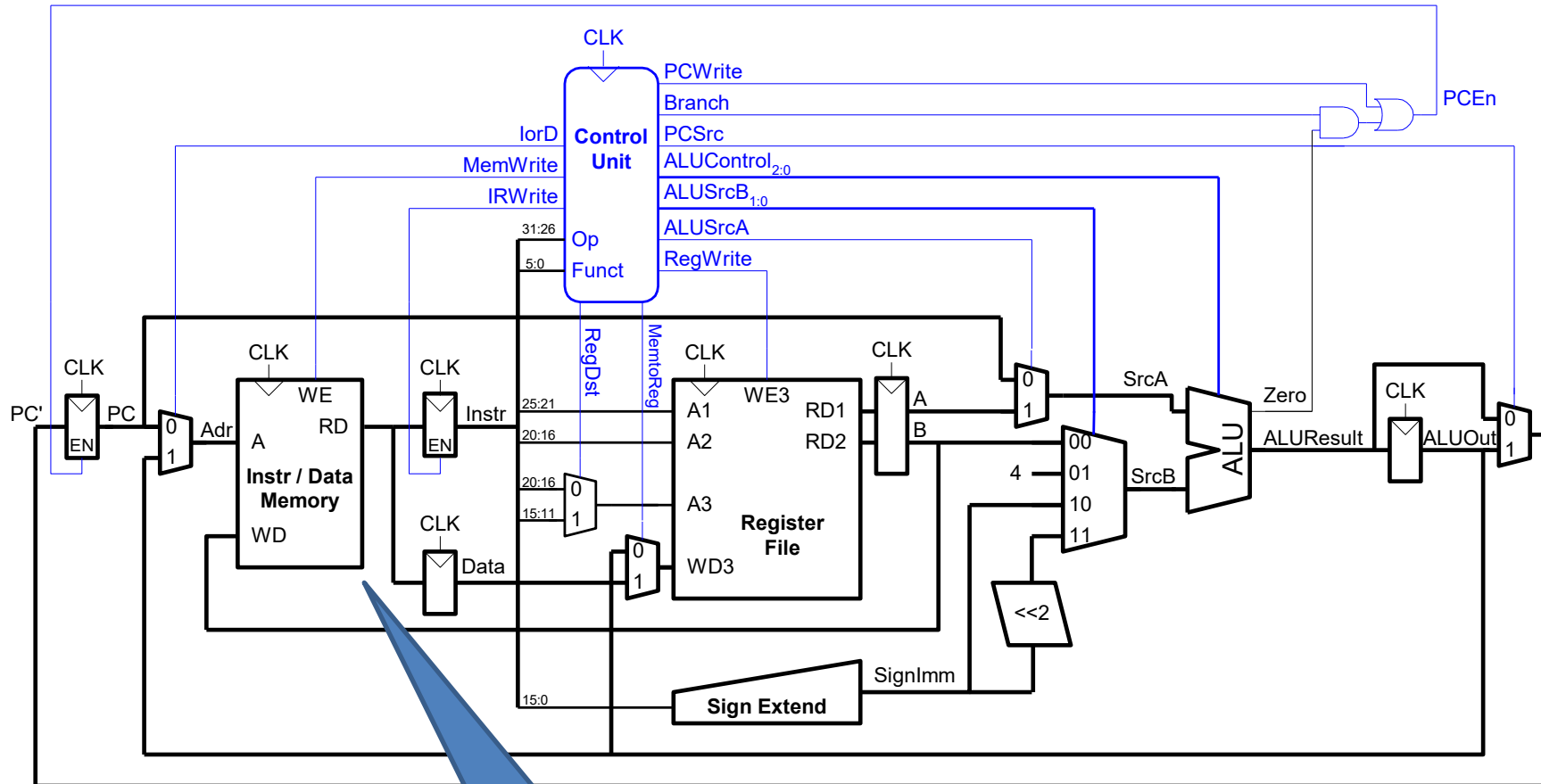


Memory is NOT
part of the
processor

Multicycle Processor Architecture

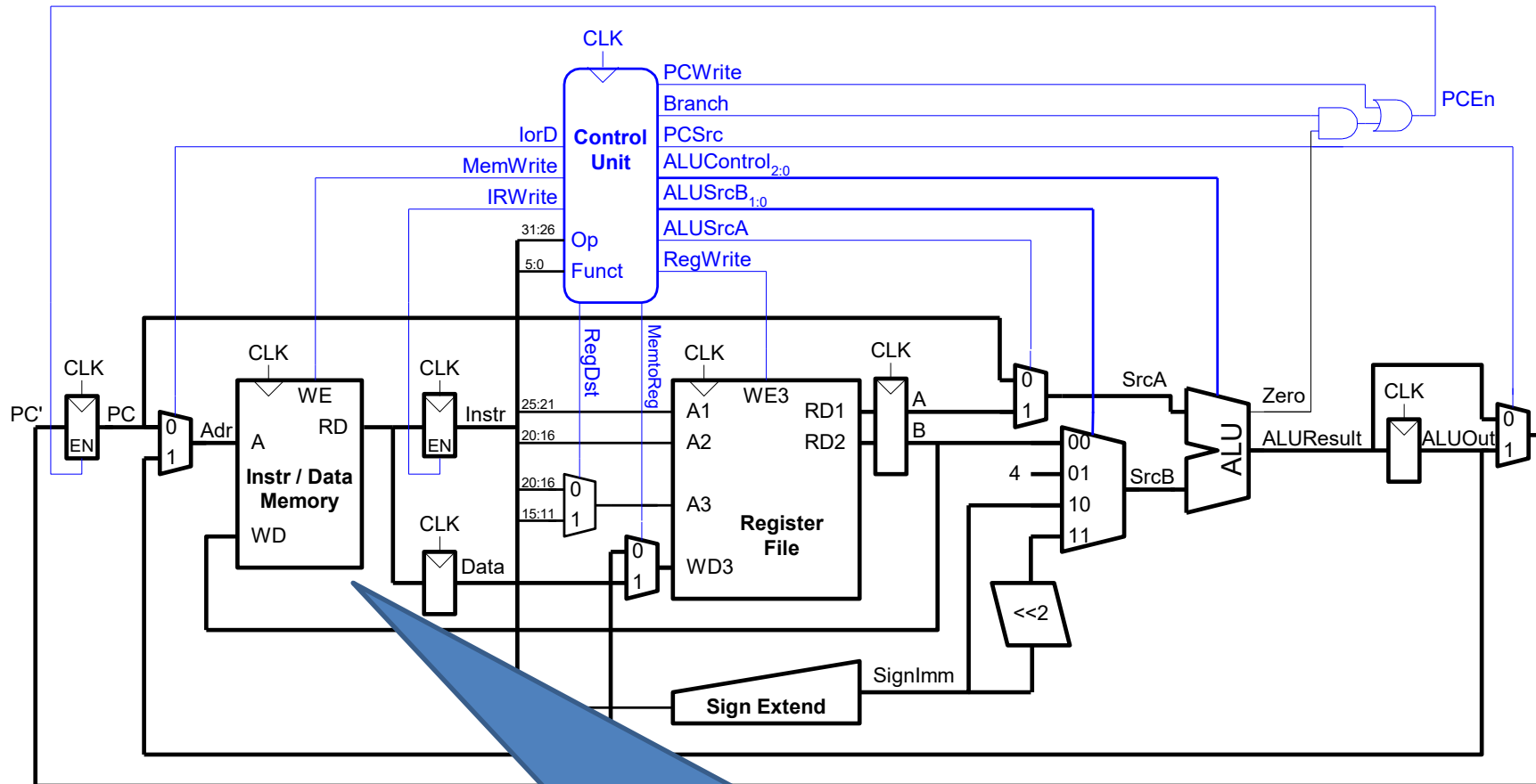


The memory works at each clock cycle, executing a read or write operation, depending on WE.

Multicycle Processor Architecture

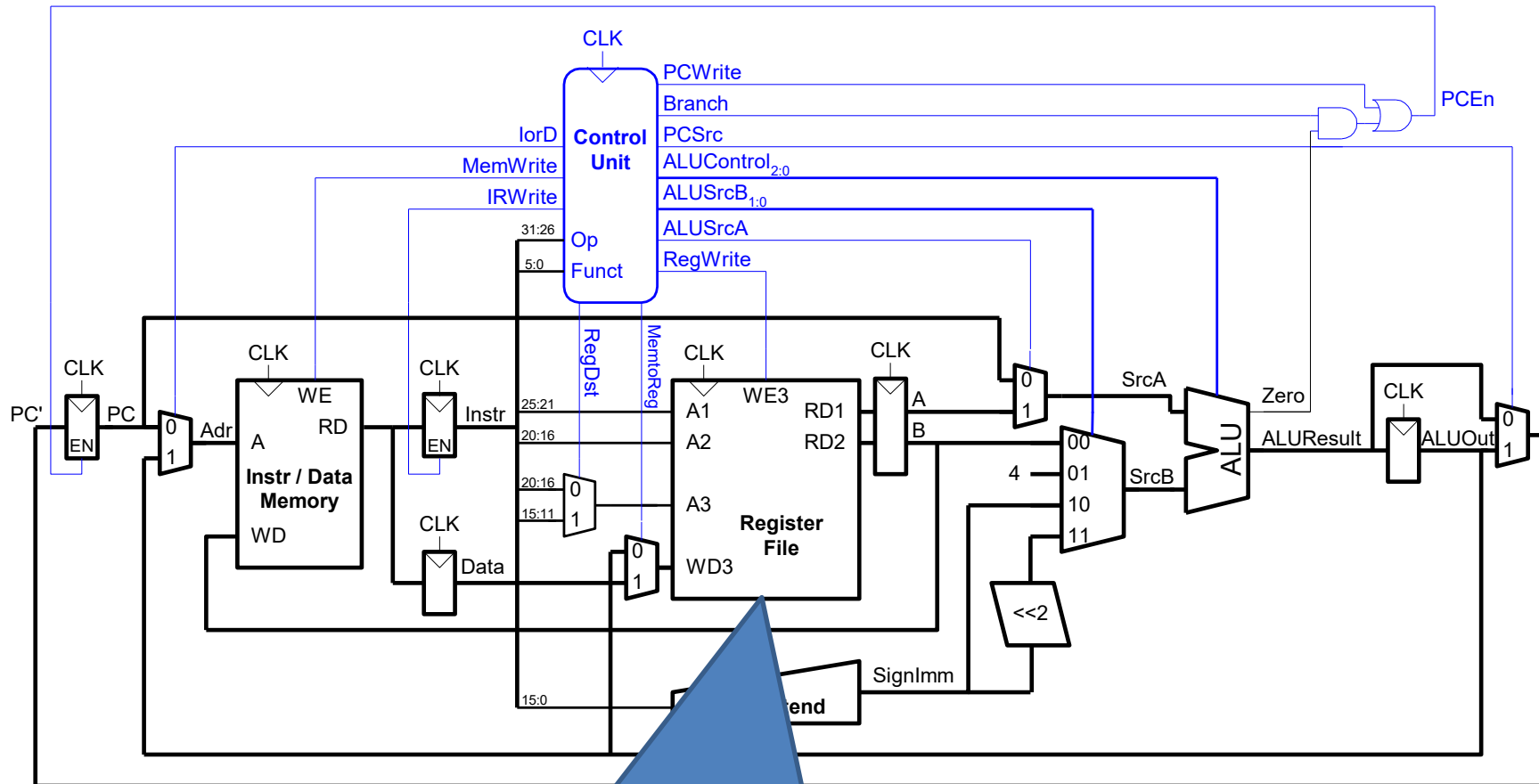

The RF works at each clock cycle, executing a read of two values or a write operation, depending on WE3.

Multicycle Processor Architecture

 


All registers work at each clock cycle, storing the value on their inputs, if not disabled.

MIPS Processor

- Consider subset of MIPS instructions:
 - R-type instructions: `and`, `or`, `add`, `sub`, `slt`
 - Memory instructions: `lw`, `sw`
 - Branch instructions: `beq`

MIPS Processor Multicycle

 - Multiple-cycle CPU
 - Only one stage of instruction per clock cycle
 - The clock is made as long as the slowest stage




MIPS State Elements

- Determines everything about the execution status of a processor
 - PC register
 - Instruction and Data memory
 - Instruction and Data registers
 - Register file
 - Operand registers
 - Result register
- For these state elements, clock is used for write but not for read
 - Asynchronous read, Synchronous write

Multicycle Datapath: Instruction Fetch


STEP 1: Send address to memory

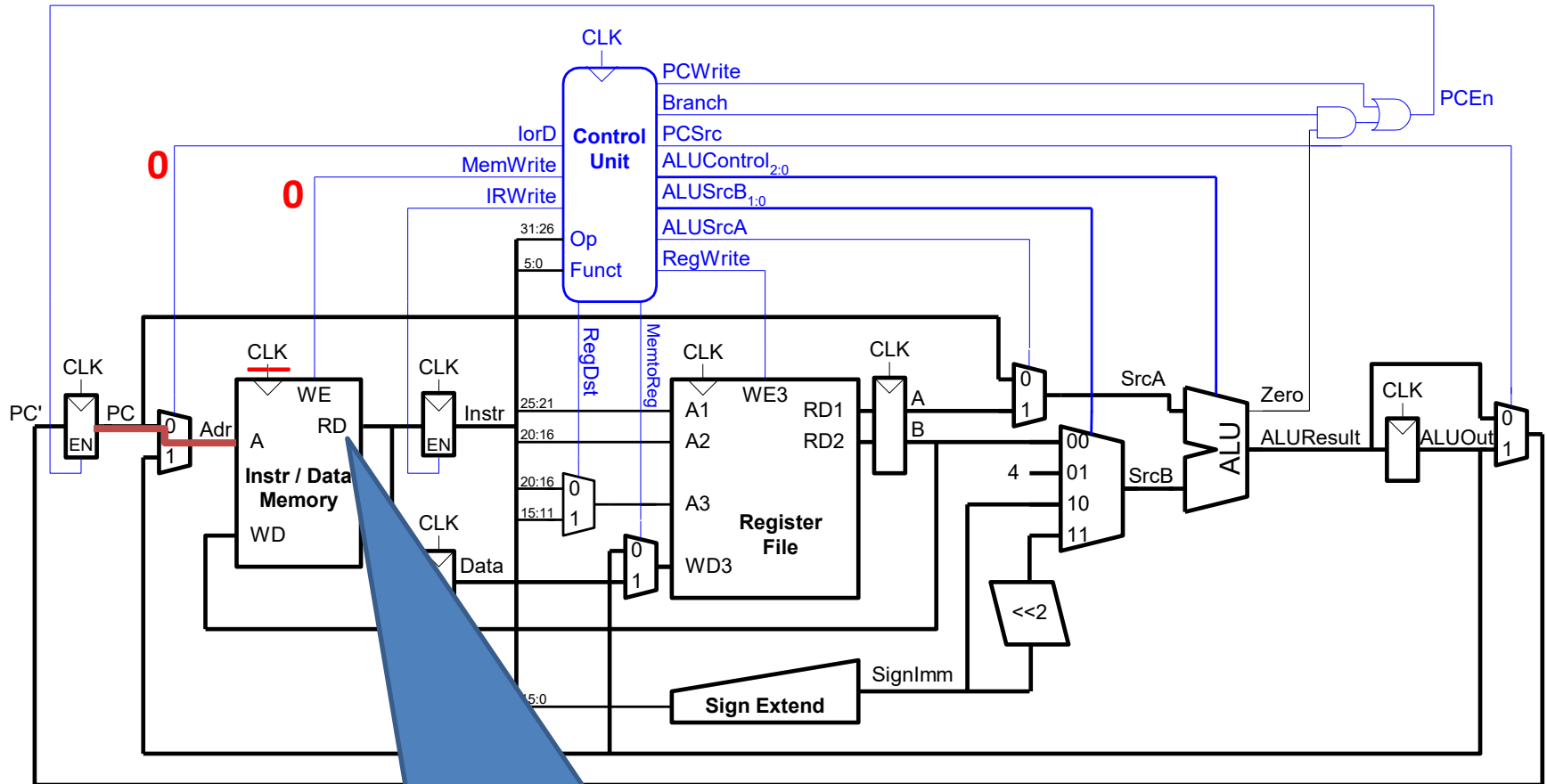

CLK: writing data on RD.

Multicycle Datapath: Instruction Fetch

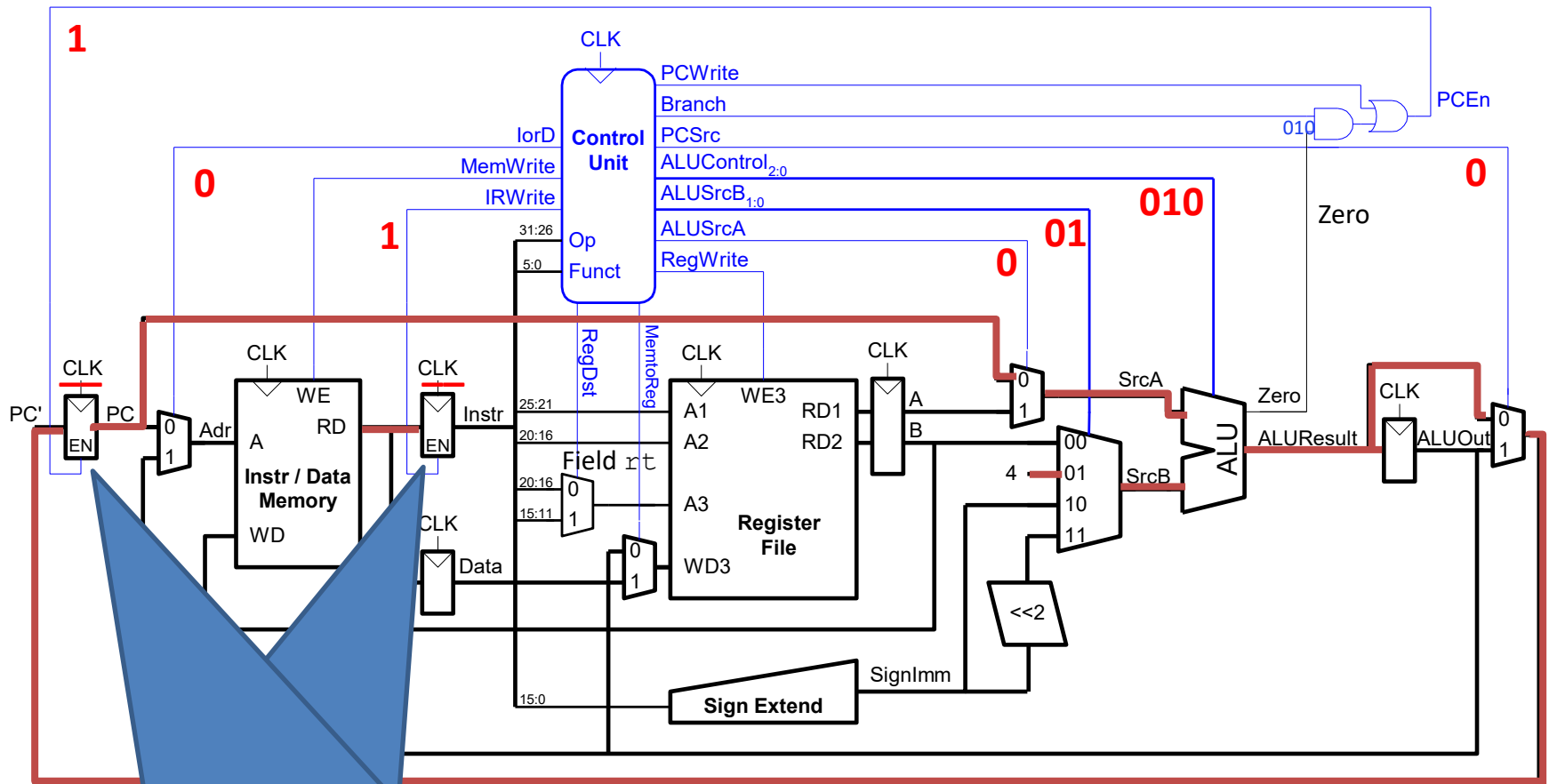
STEP 2: Write instruction into IR and update PC



CLK: writing RD on IR. Update PC

Multicycle Datapath: lw


STEP 3a: Read rs from Register File

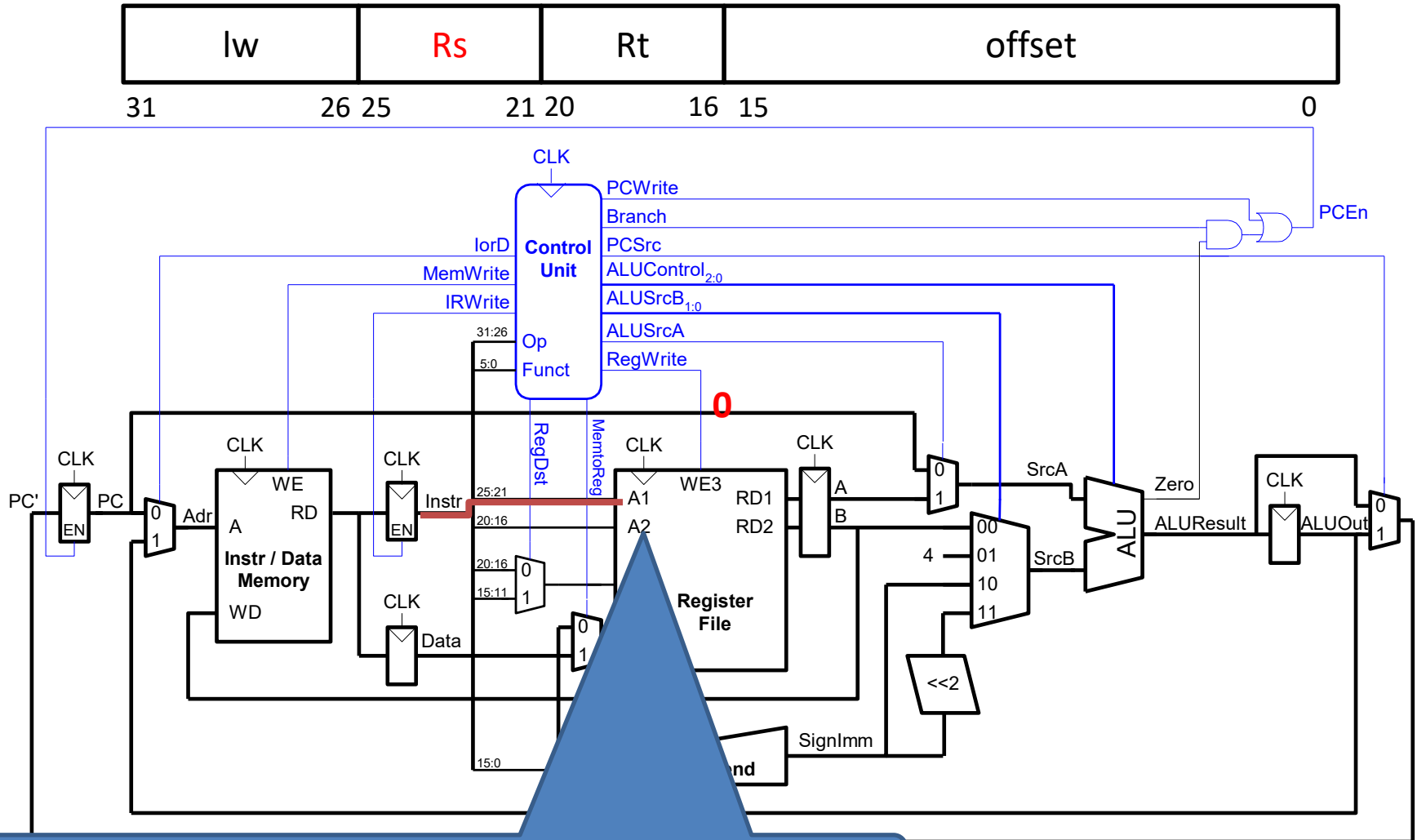

Asynchronous read of the register file

Multicycle Datapath: lw


STEP 3b: Sign-extend the immediate

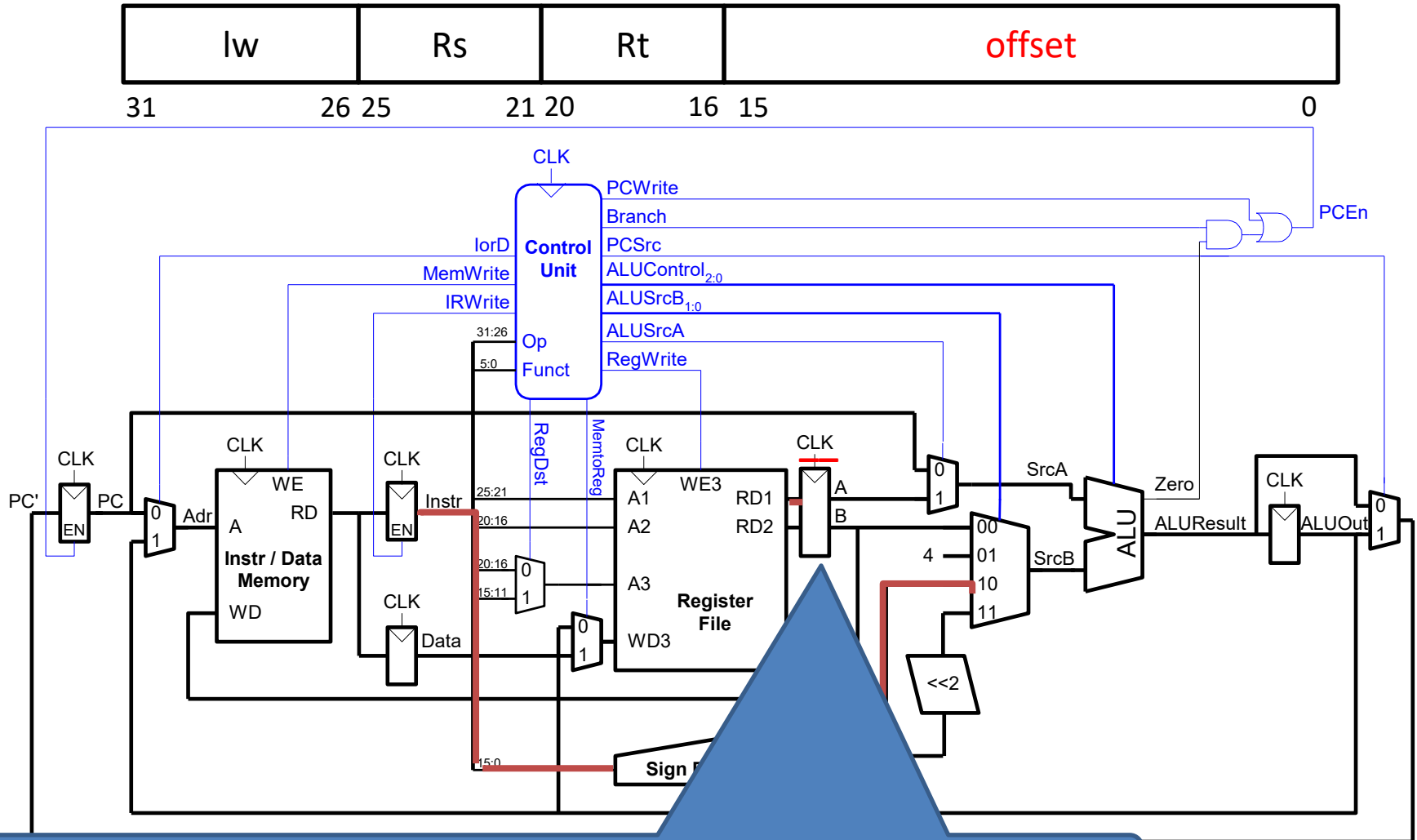

CLK: writing RD1 into the operand register A

Multicycle Datapath: 1_w


STEP 4: Compute the memory address

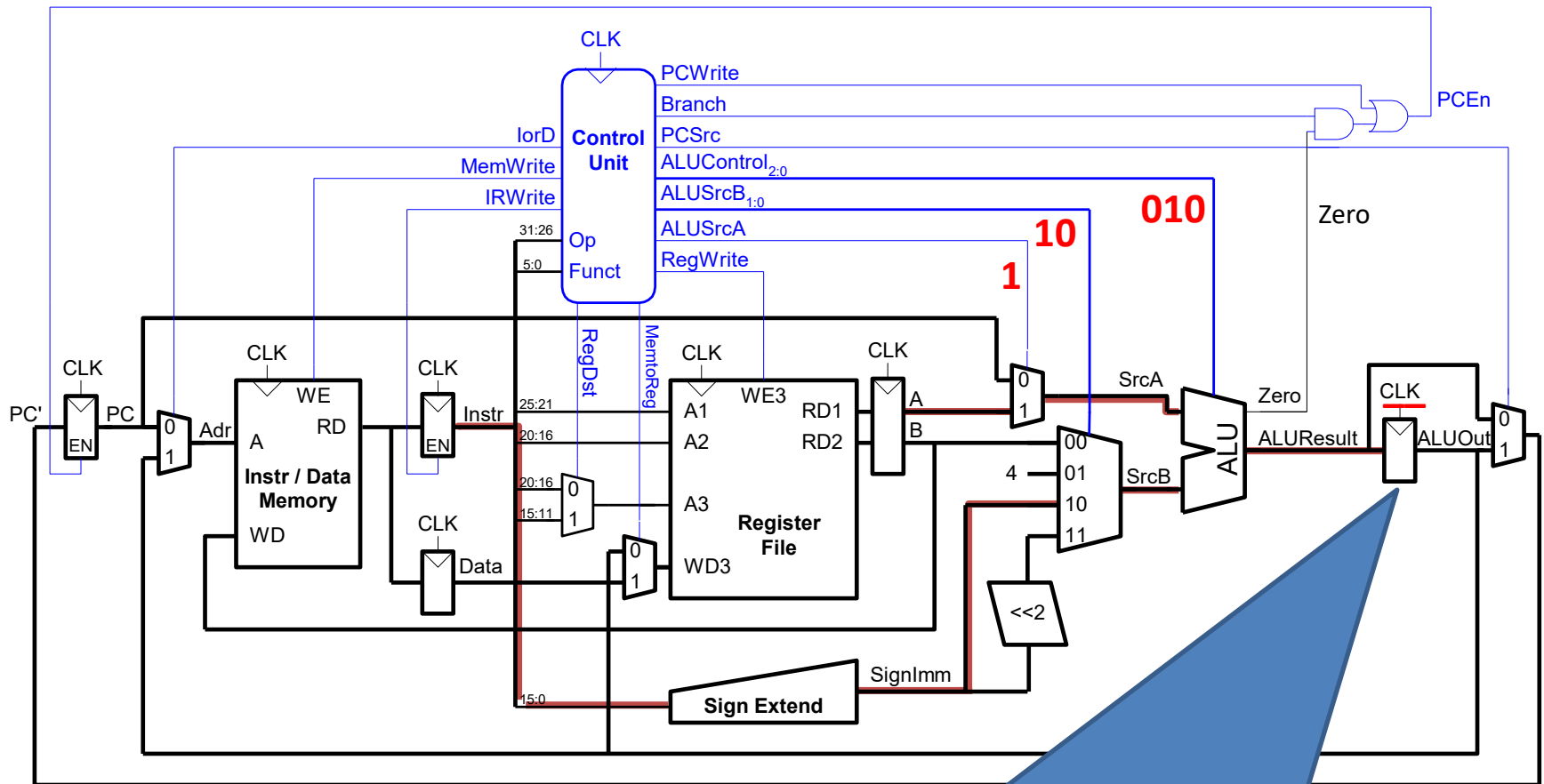

CLK : writing into the result register

Multicycle Datapath: 1_w


STEP 5: Send address to memory

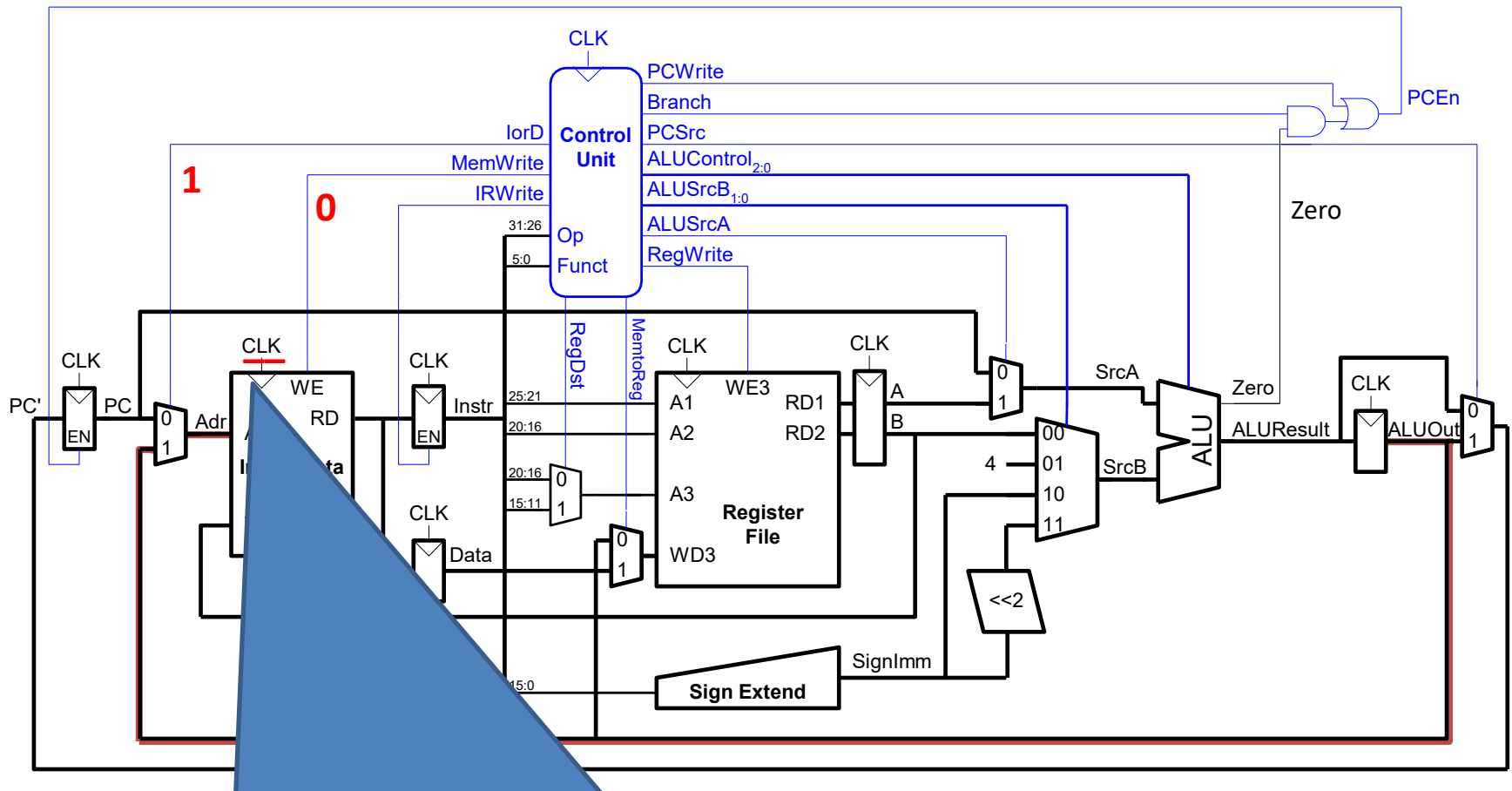

CLK : writing the computed address into the memory interface Address Register.

Multicycle Datapath: 1_W


STEP 6: Read data from memory

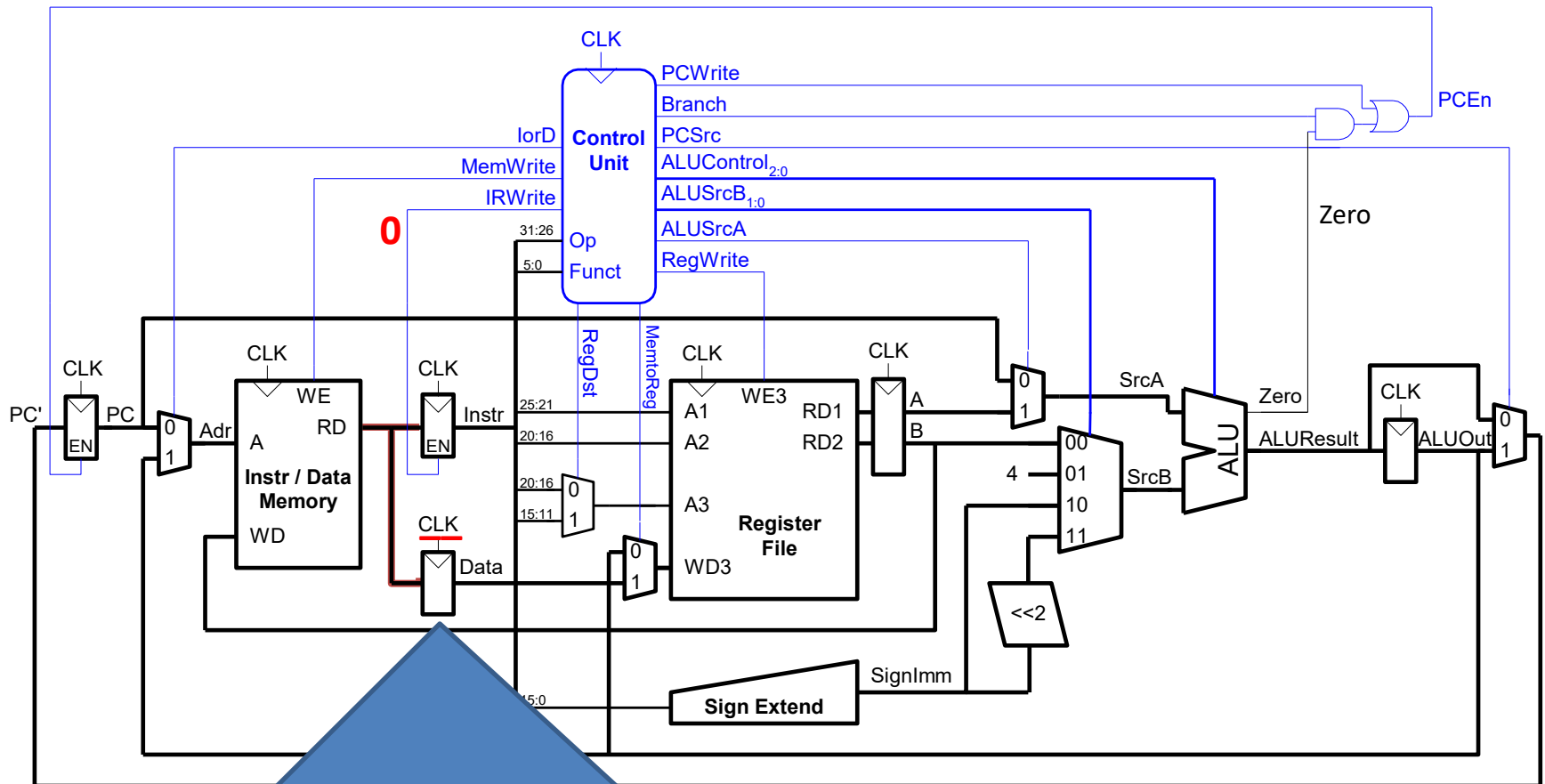

CLK : writing the RD value into the Data Register.

Multicycle Datapath: \perp_w

STEP 7: Write data back to register file

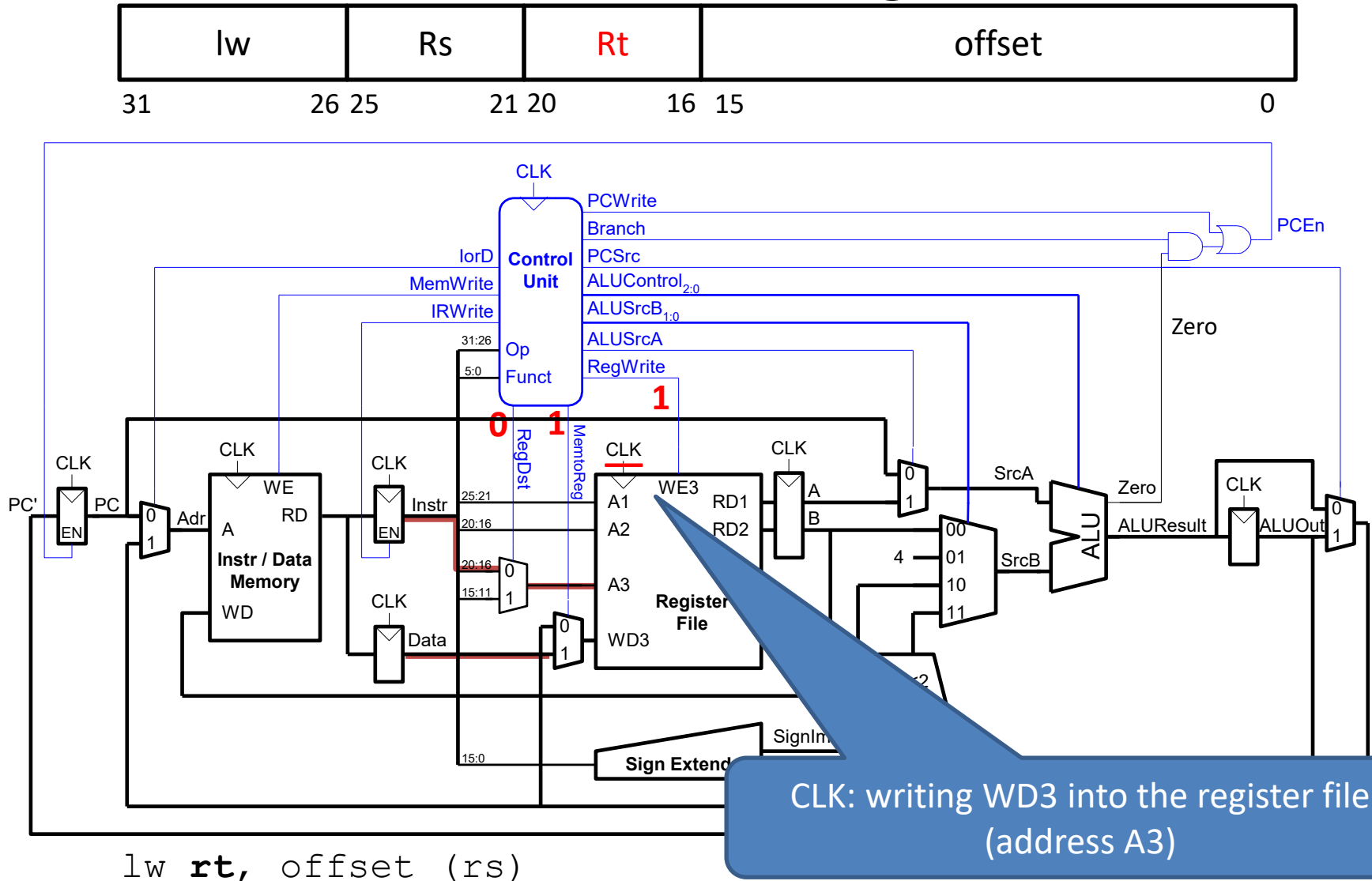

Multicycle Datapath: sw


Write data in rt to memory

`sw rt , offset (rs)`

Steps 1 and 2 as in previous example


Multicycle Datapath: SW

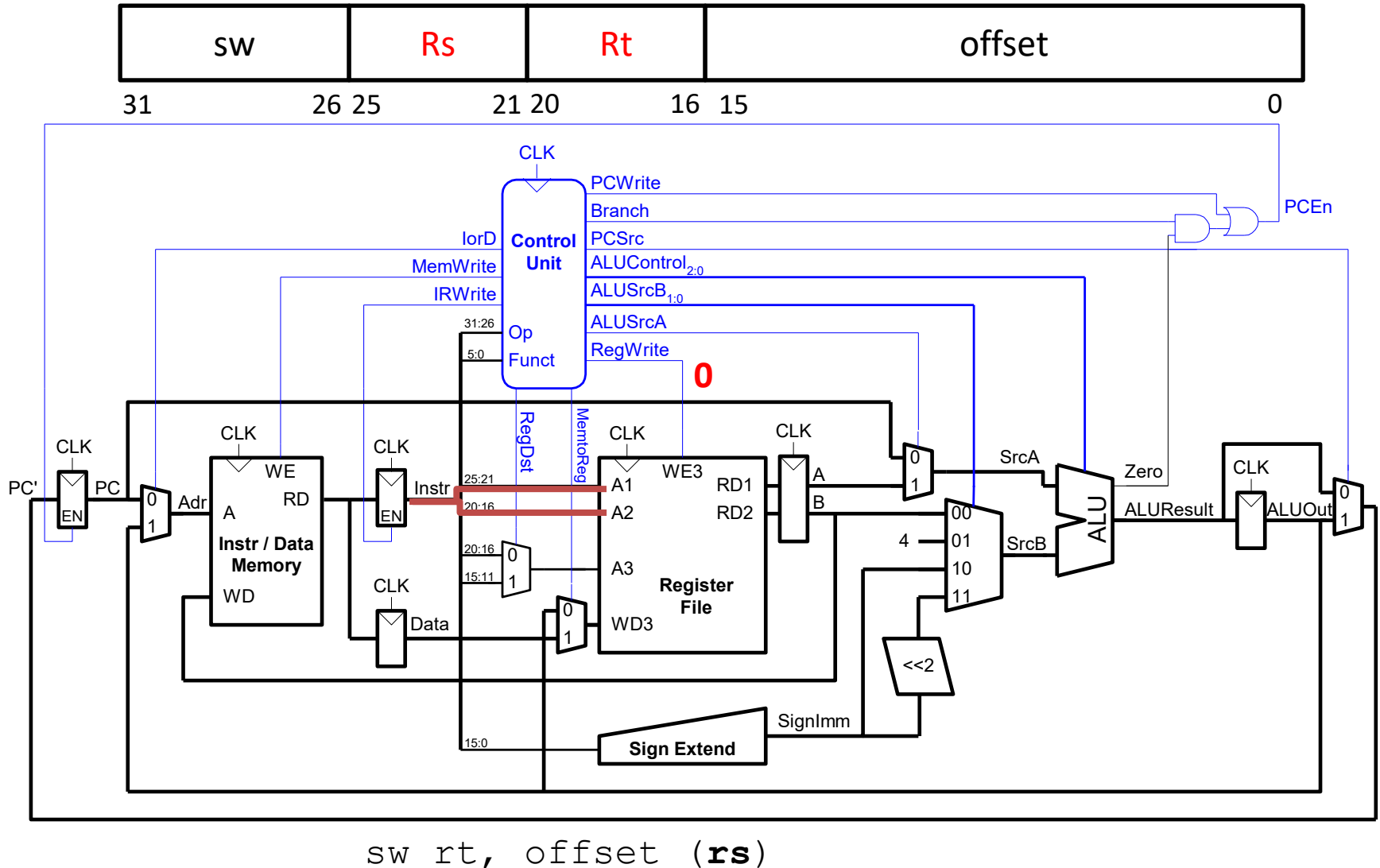STEP 3a: Read rs and rt from Register File




Multicycle Datapath: SW

STEP 3b: Sign-extend the immediate

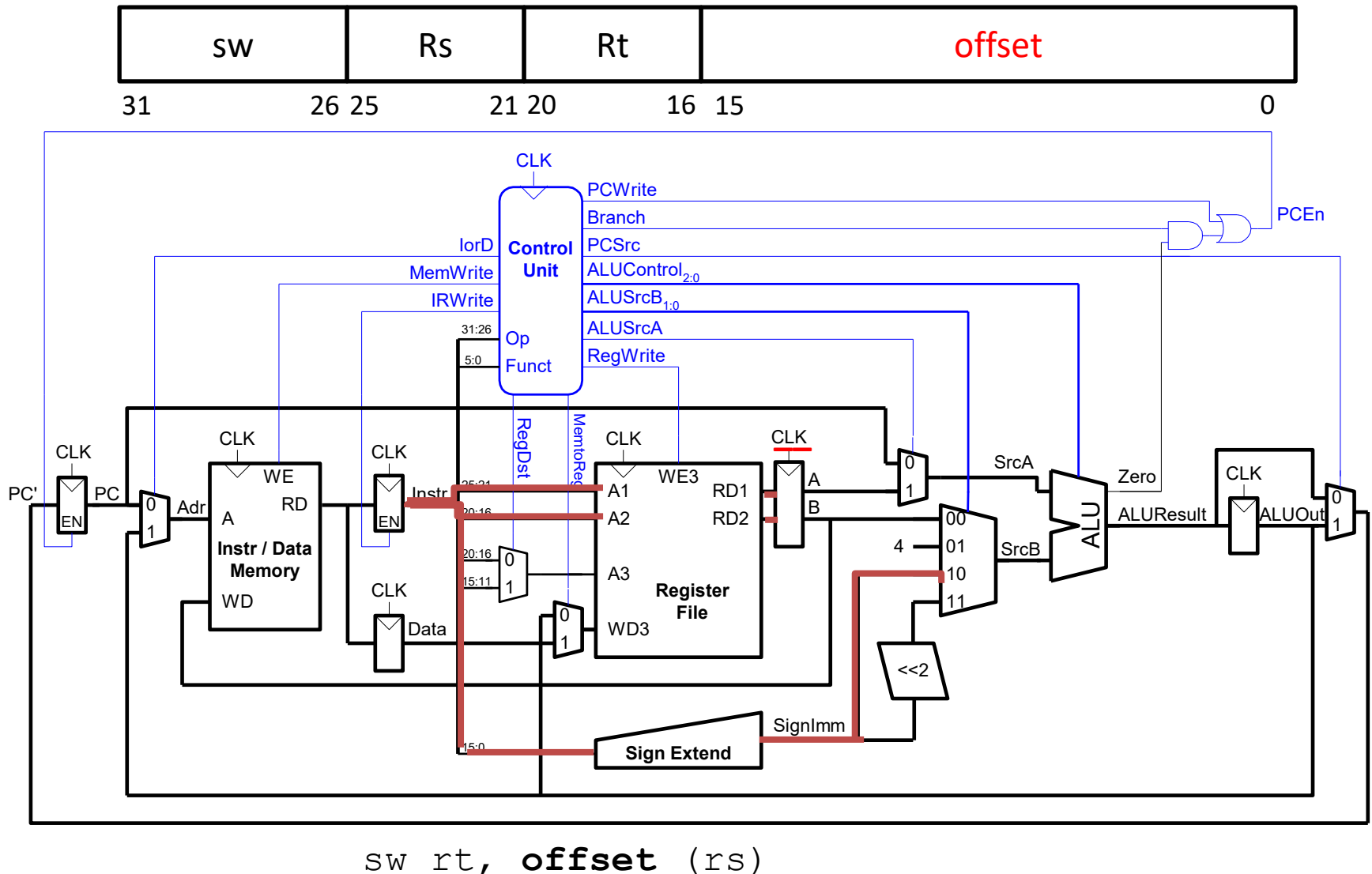


Multicycle Datapath: SW

STEP 4: Compute the memory address

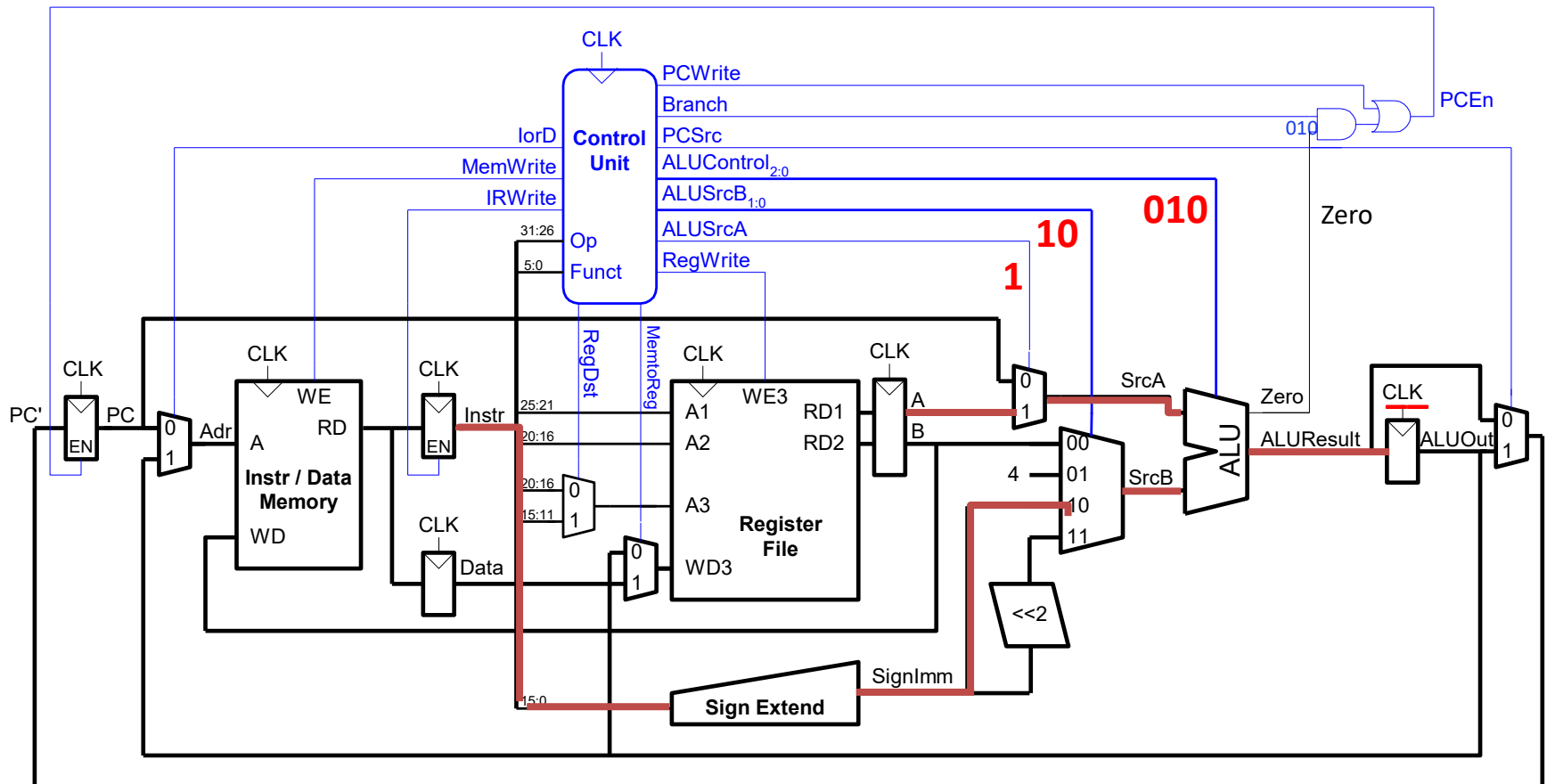


Multicycle Datapath: SW

STEP 5a: Send address to memory

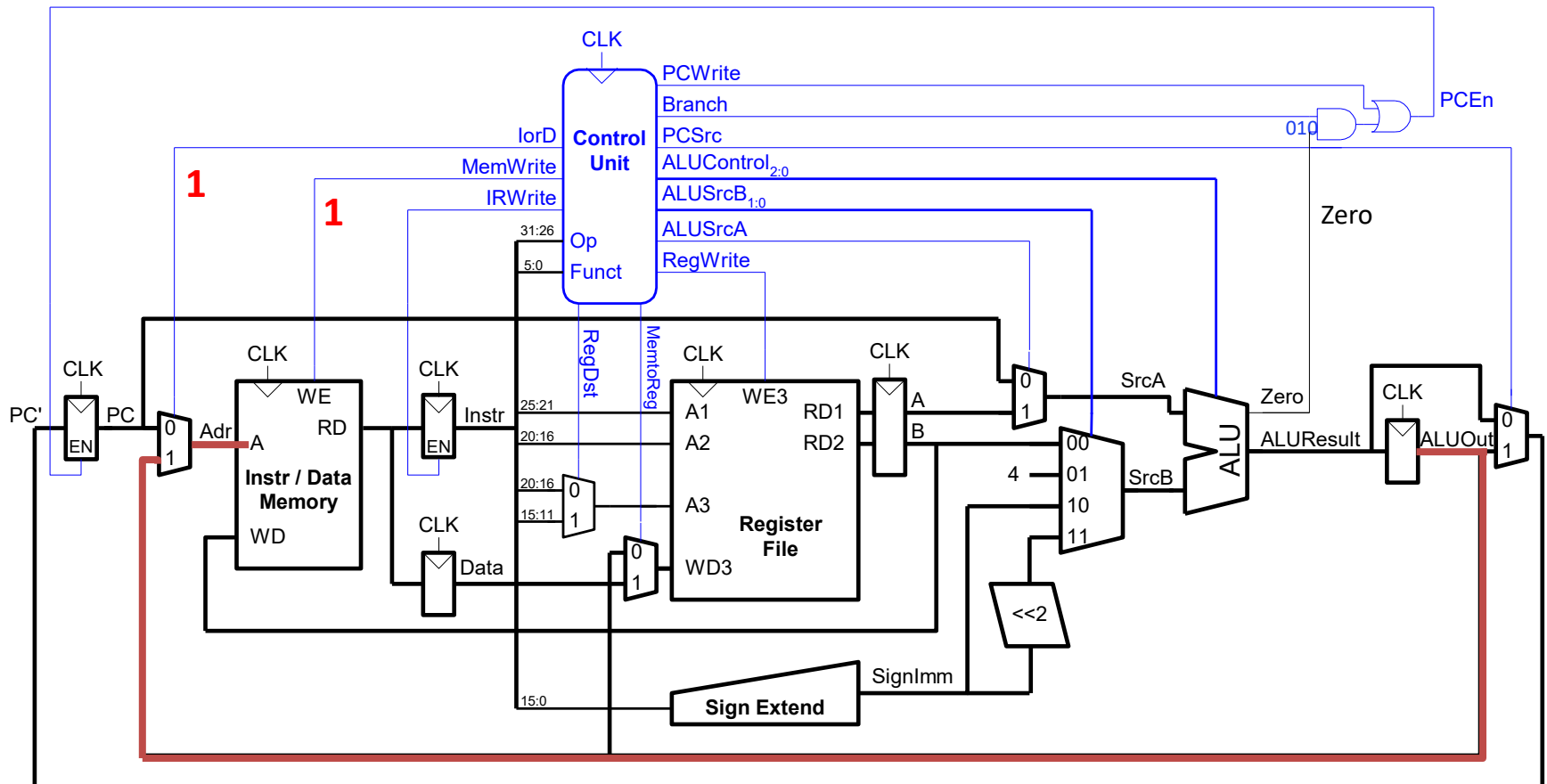

Multicycle Datapath: SW

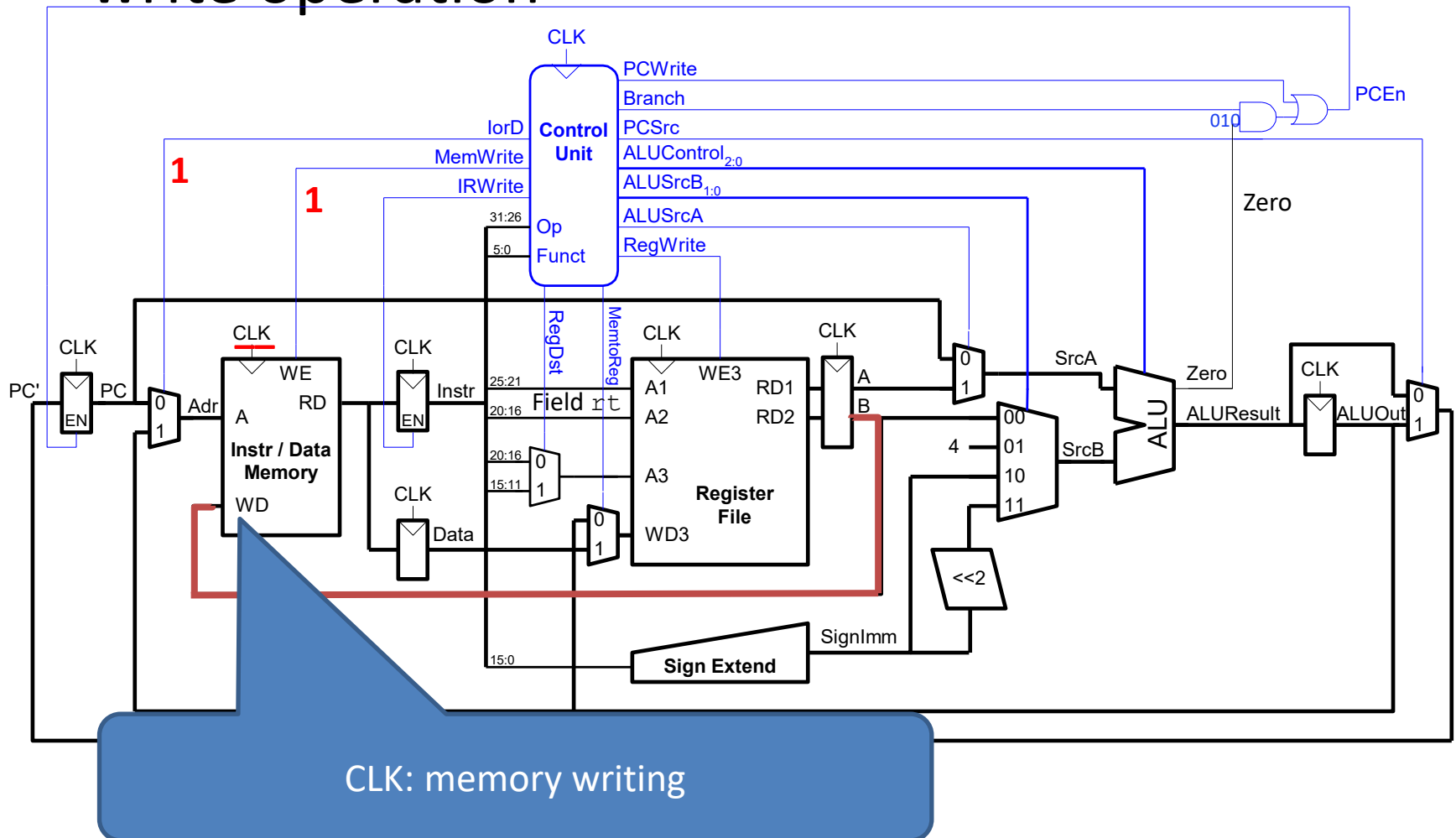STEP 5b: Send data to memory and activate write operation





Multicycle Datapath: R-Type instr

- Read from `rs` and `rt`
`add rd, rs, rt`
- Write *ALUResult* to register file
- Write to `rd` (instead of `rt`)
- Steps 1 and 2 as in previous examples

Multicycle Datapath: R-Type instr

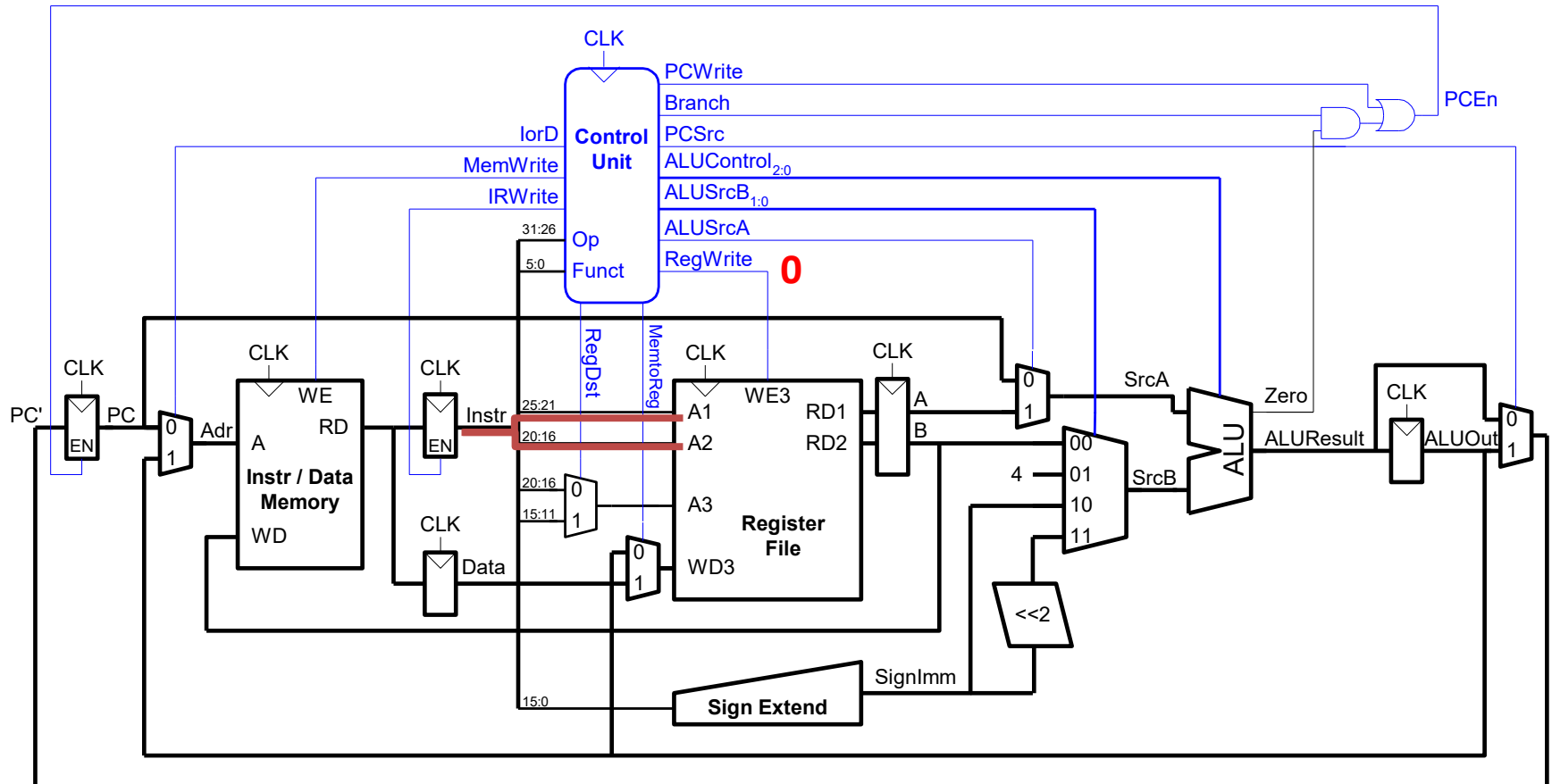 
STEP 3: Read source operands from Register File



add rd, rs, rt

Multicycle Datapath: R-Type instr


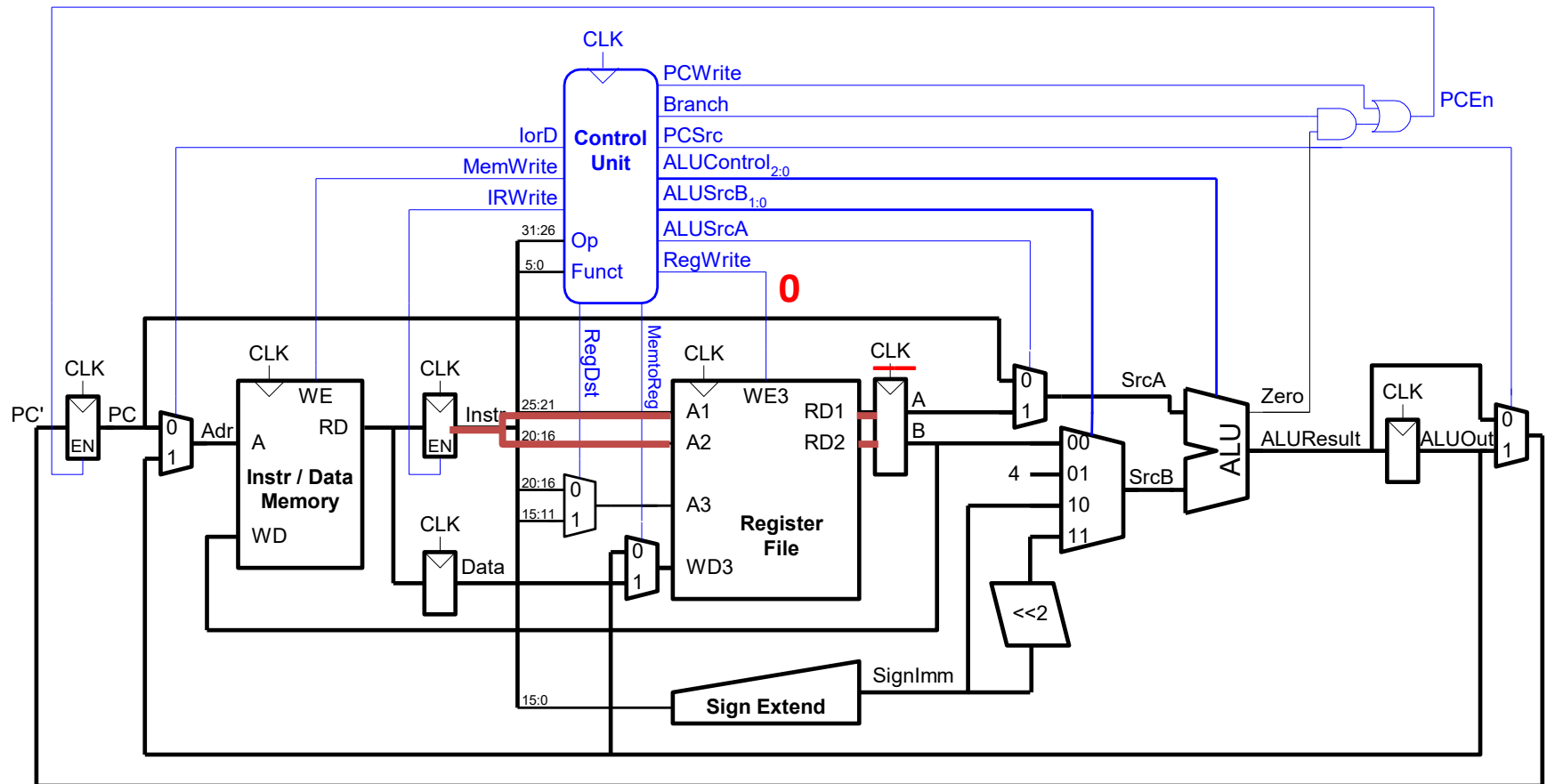
STEP 3b: Write source operands into Register A/B



add rd, rs, rt



Multicycle Datapath: R-Type instr

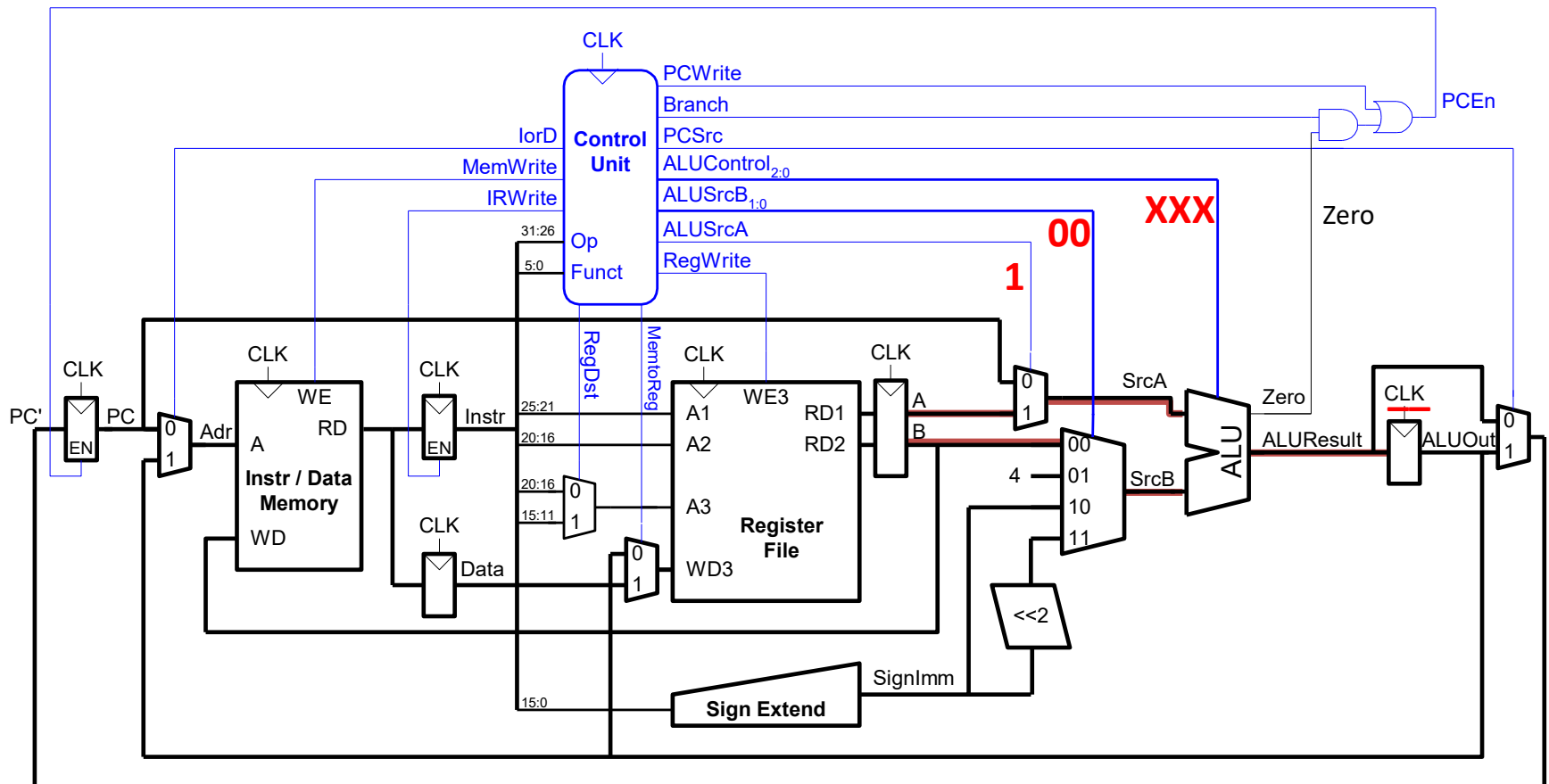 STEP 4: Perform the required ALU operation



Multicycle Datapath: R-Type instr

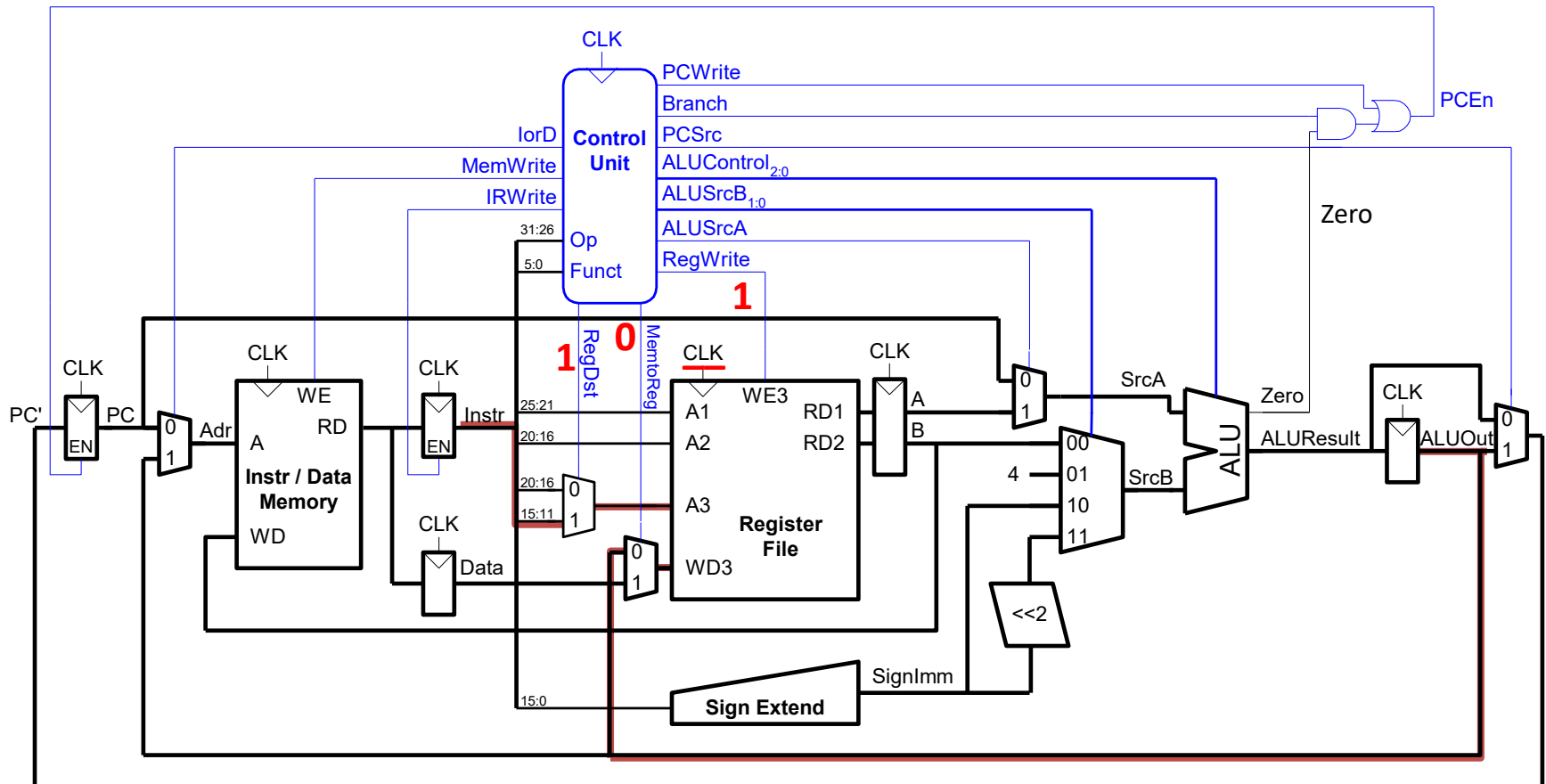 STEP 5: Send result to Register File (Rd)




Multicycle Datapath: beq

beq rs, rt, lab

- $rs == rt?$
- $BTA = (\text{sign-extended immediate} \ll 2) + (PC+4)$
- Steps 1 and 2 as in previous examples


Multicycle Datapath: beq

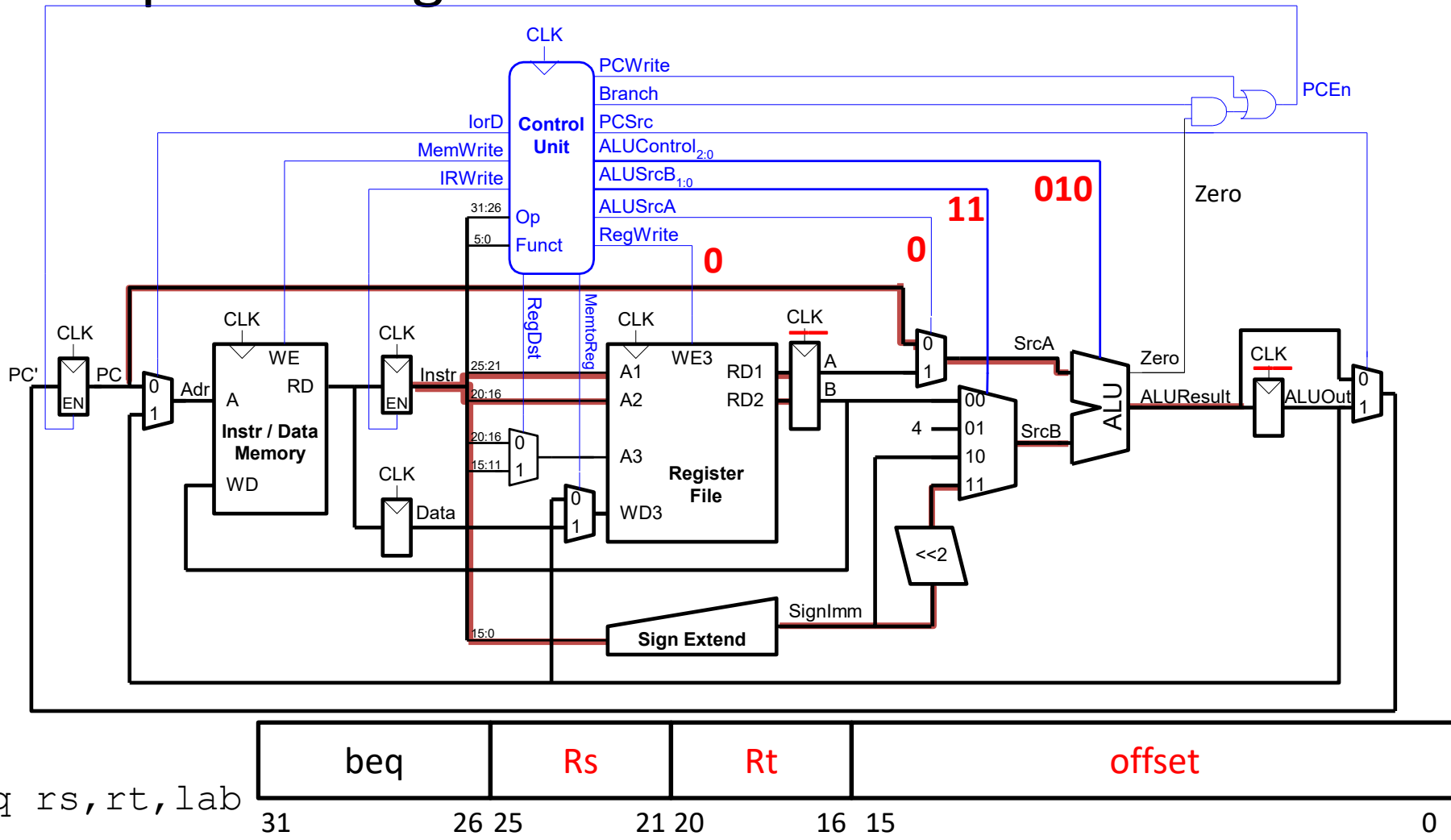STEP 3: compute the new PC value / read the 2 operand registers from RF



Multicycle Datapath: beq

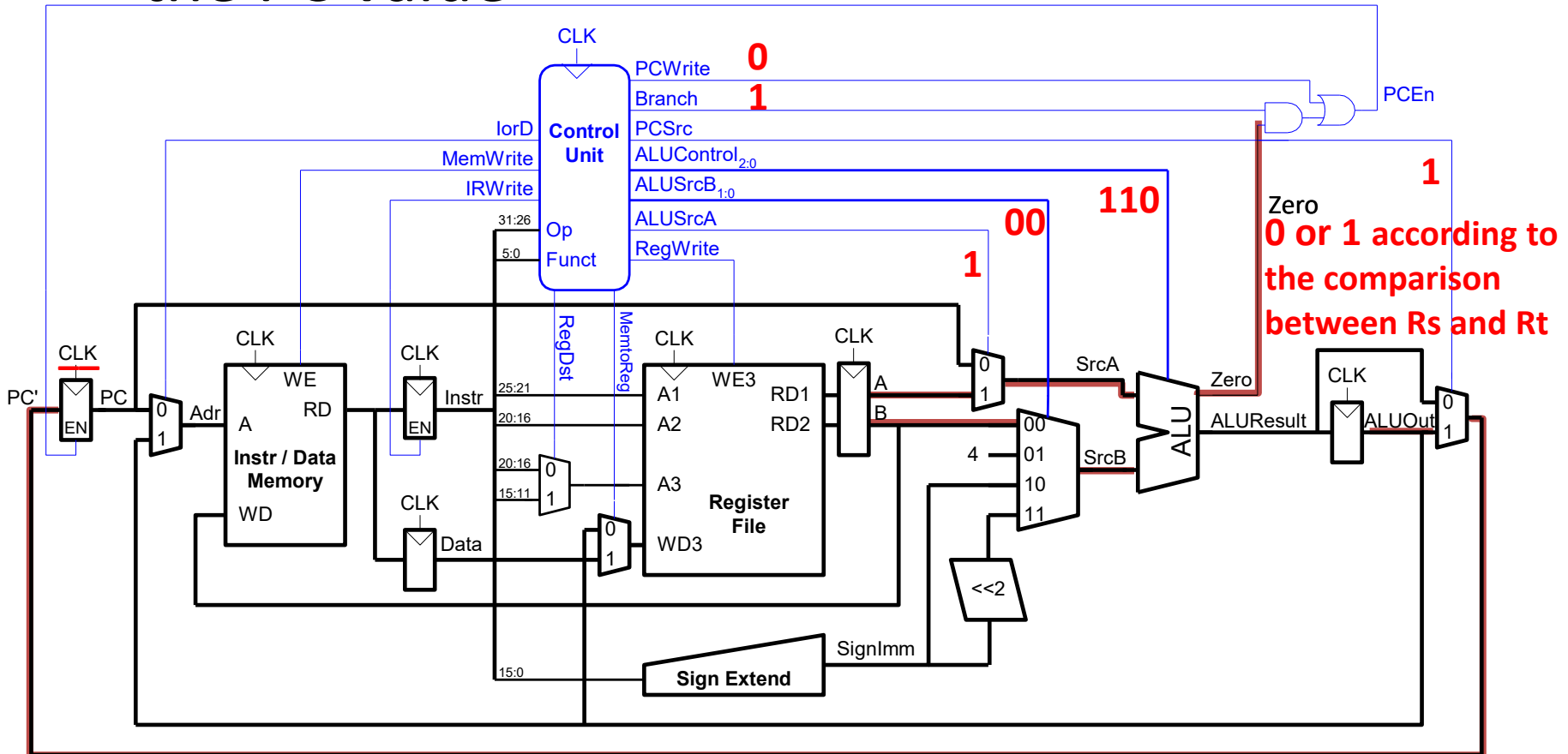STEP 4: compare the 2 operands and update the PC value




`beq rs, rt, lab`


Multicycle Datapath: j

- $\text{BTA} = (\text{jump address field} \ll 2)_{[27:0]}$ combined with $(\text{PC}+4)_{[31:28]}$
- Steps 1 and 2 as in previous examples

Multicycle Datapath+CU: j

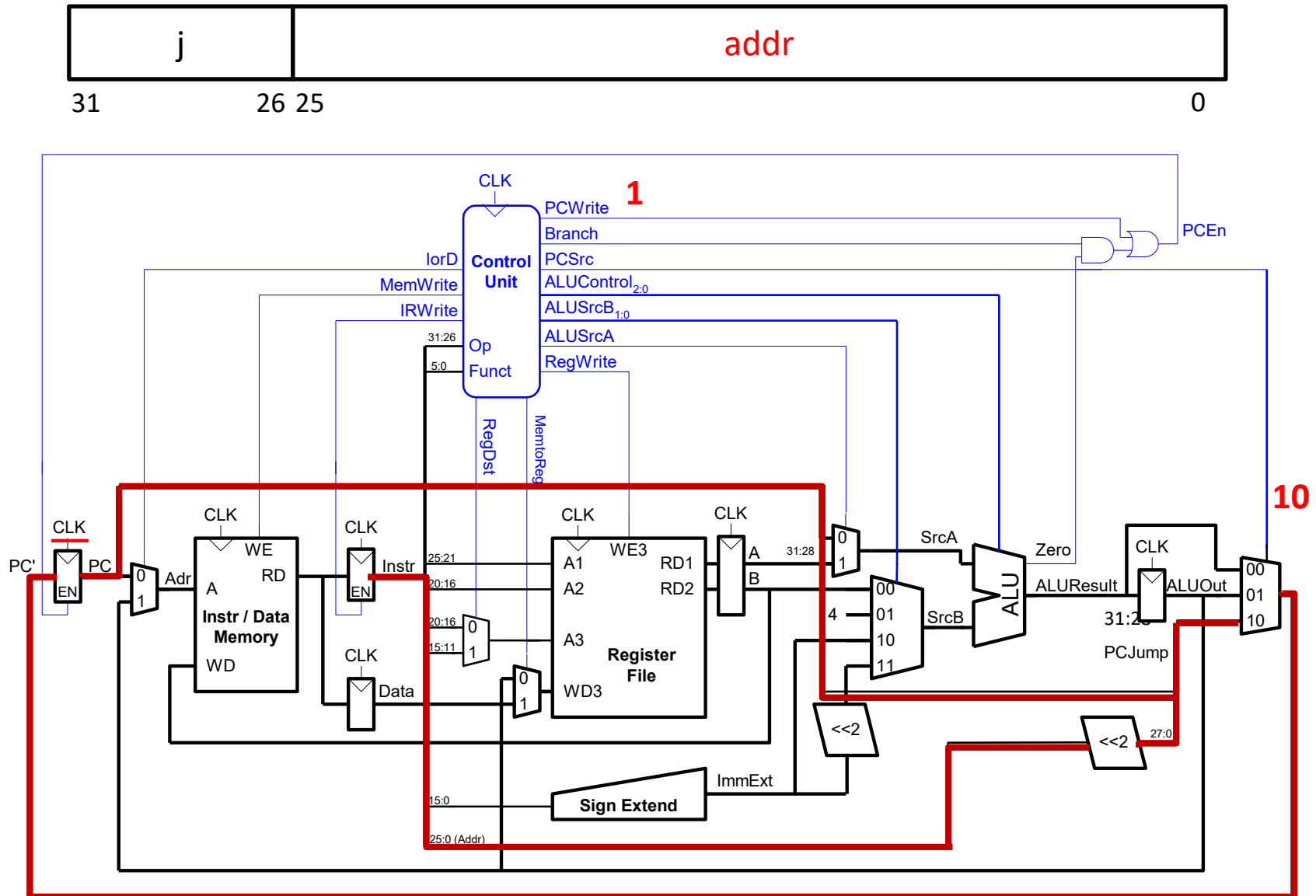

Multicycle Control

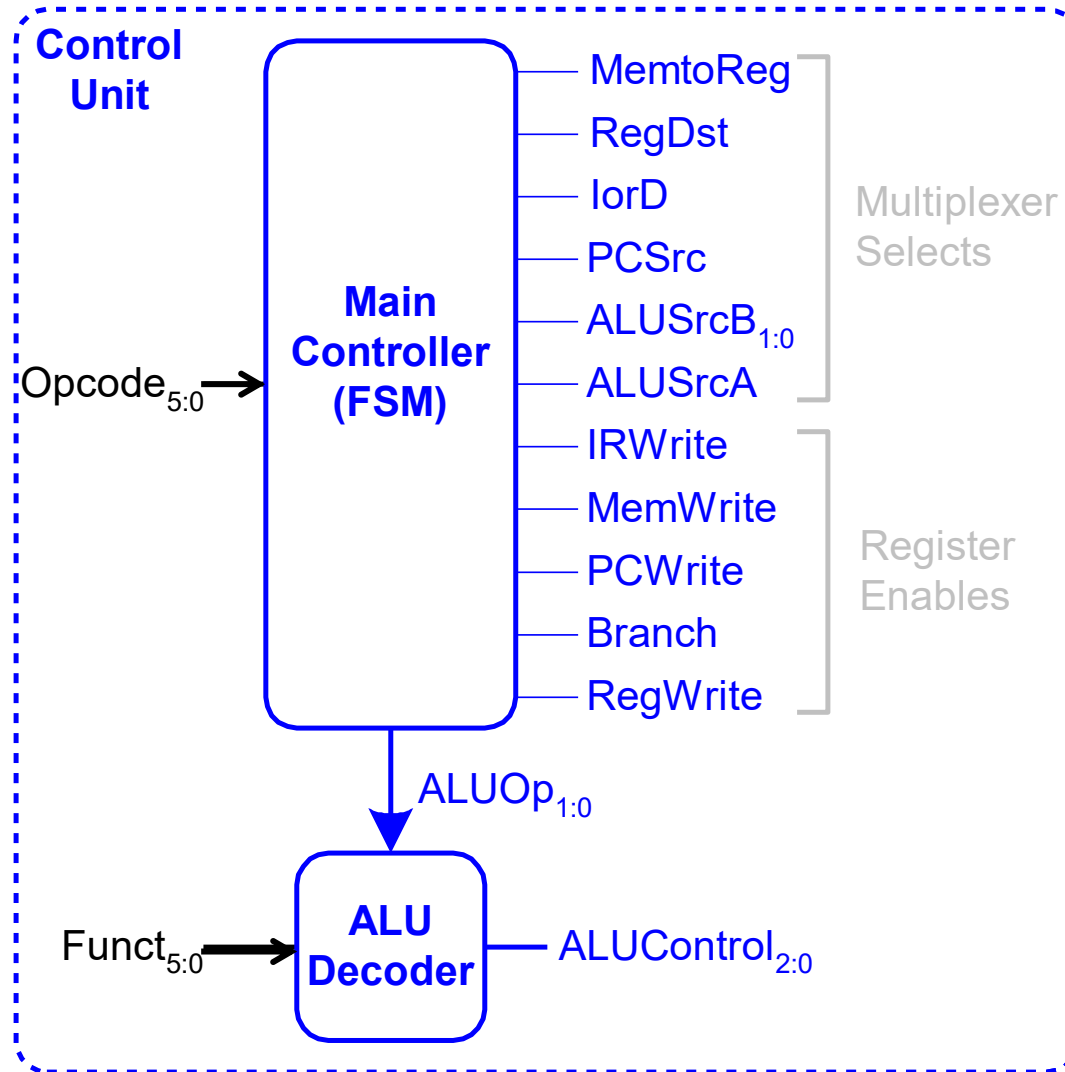


Control Unit: ALU Decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at Funct
11	Not Used

ALUOp _{1:0}	Funct	ALUControl _{2:0}
00	X	010 (Add)
X1	X	110 (Subtract)
1X	100000 (add)	010 (Add)
1X	100010 (sub)	110 (Subtract)
1X	100100 (and)	000 (And)
1X	100101 (or)	001 (Or)
1X	101010 (slt)	111 (SLT)


Main Controller FSM: Fetch

 1. Send the PC to memory
2. Read the instruction from memory and update PC




Main Controller FSM: lw

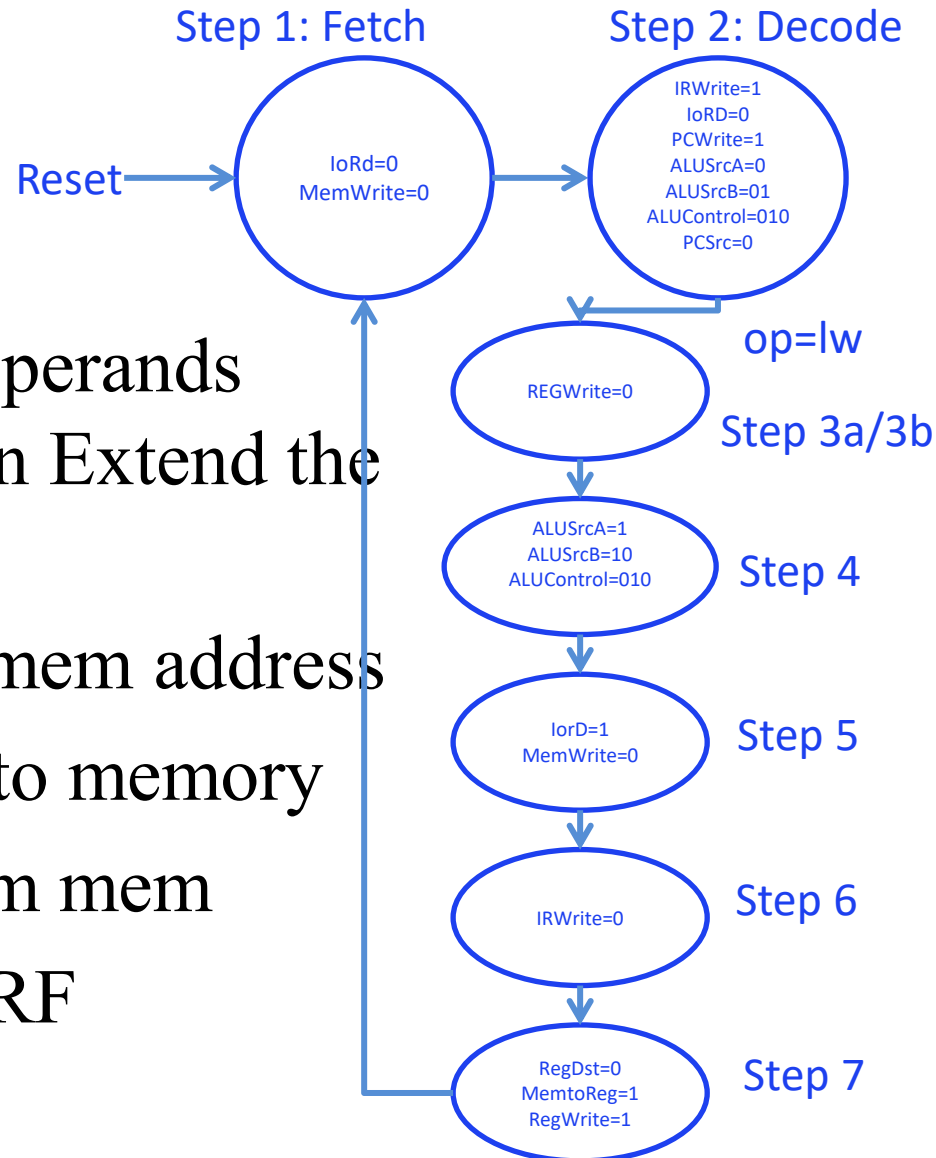3. Read source operands from RF / Sign Extend the Immediate
4. Compute the mem address
5. Send address to memory
6. Read data from mem
7. Write data to RF




Main Controller FSM: S_W

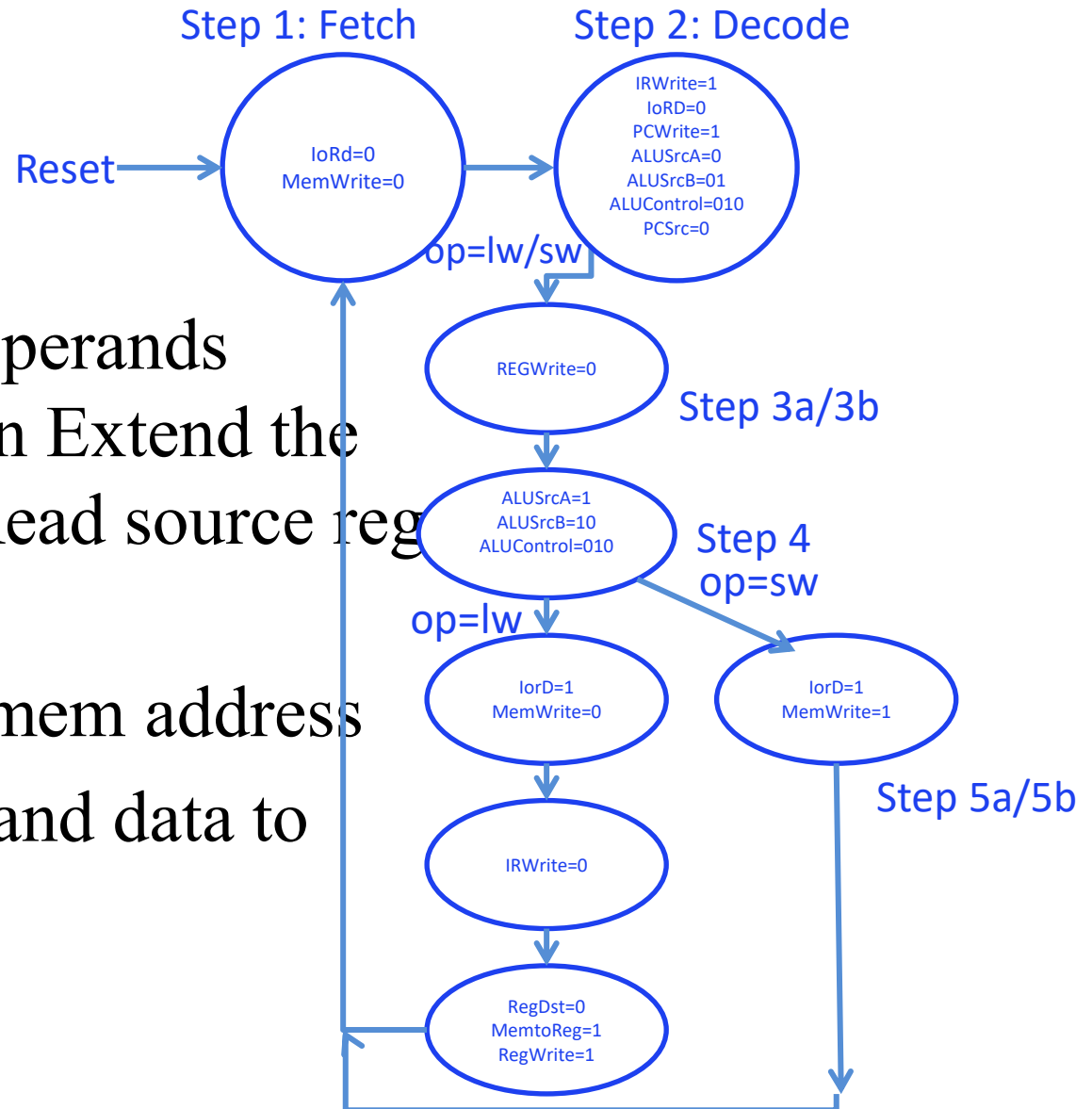3. Read source operands from RF / Sign Extend the Immediate / Read source reg from RF
4. Compute the mem address
5. Send address and data to memory



Main Controller FSM: R-type

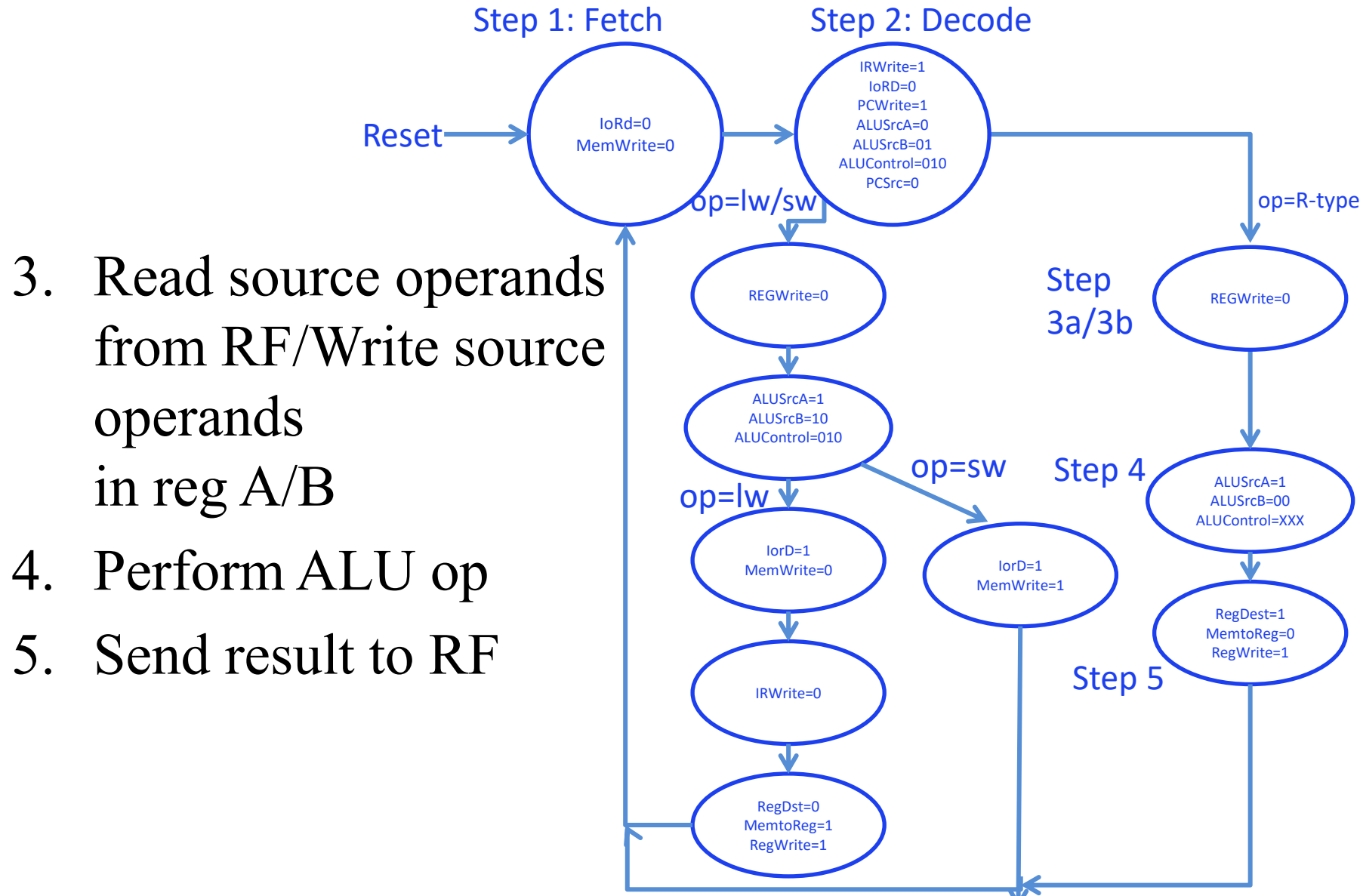

Processor Performance

- Program execution time

Execution Time =
 $(\text{\#instructions})(\text{cycles/instruction})(\text{seconds/cycle})$

- Definitions:
 - CPI: cycles/instruction
 - clock period: seconds/cycle
- Challenge is to satisfy constraints of:
 - Cost
 - Power
 - Performance

Multicycle Processor Performance


- Instructions take different number of cycles:
 - 3 cycles: `j`
 - 4 cycles: `beq`
 - 5 cycles: `sw`
 - 5 cycles: R-Type
 - ...
 - 7 cycles: `lw`
- CPI is weighted average
- SPECINT2000 benchmark:
 - 25% loads
 - 10% stores
 - 11% branches
 - 2% jumps
 - 52% R-type

Average CPI = $(0.02)(3) + (0.11)(4) + (0.10)(5) + \dots + (0.25)(7) = 4.12$

Multicycle Processor Performance

Multicycle critical path:
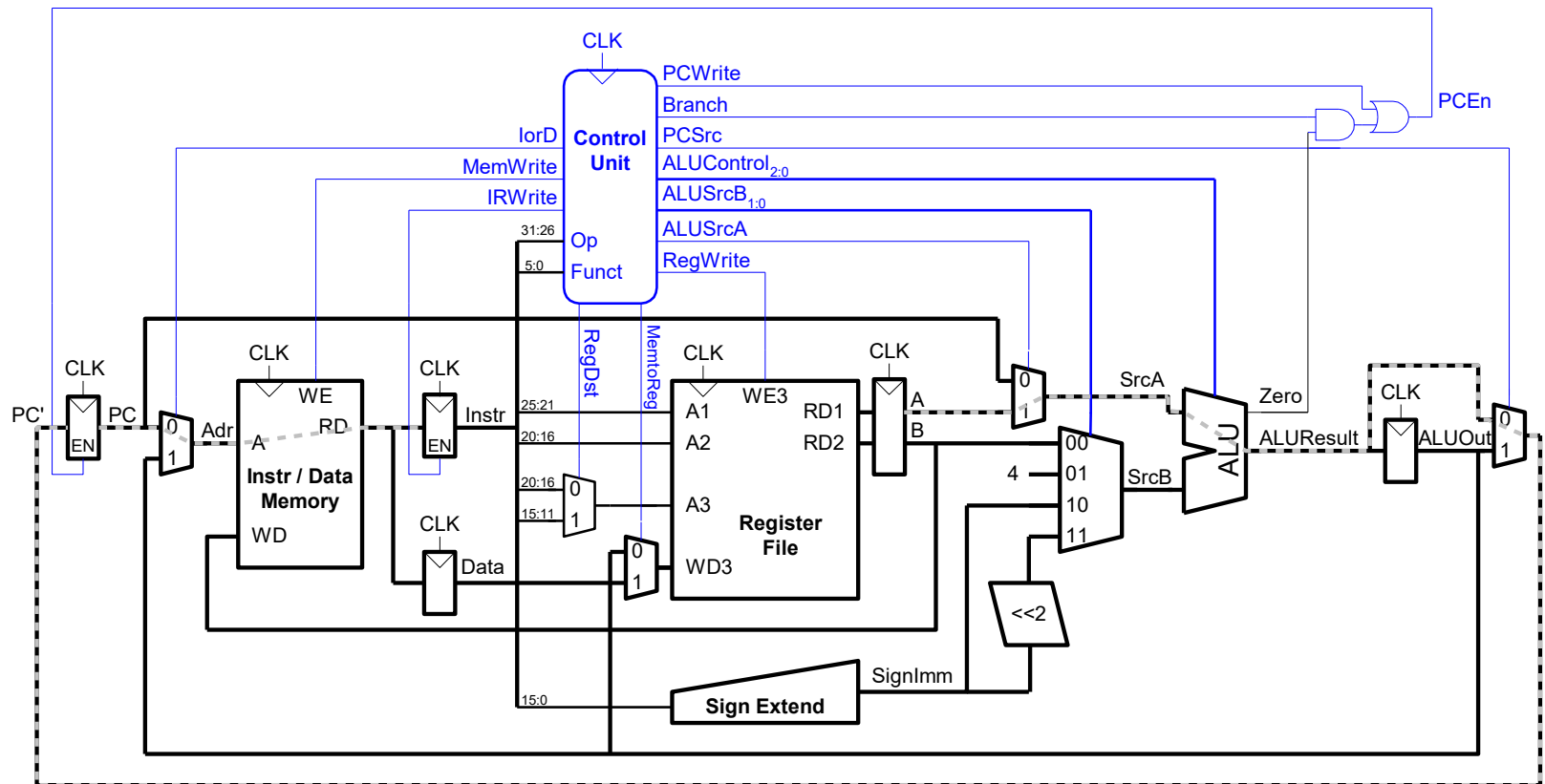
$$T_c = t_{pcq} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup}$$



Multicycle Performance Example

Element	Parameter	Delay (ps)
Register clock-to-Q	t_{pcq_PC}	30
Register setup	t_{setup}	20
Multiplexer	t_{mux}	25
ALU	t_{ALU}	200
Memory read	t_{mem}	250
Register file read	t_{RFread}	150
Register file setup	$t_{RFsetup}$	20

$$\begin{aligned}T_c &= t_{pcq_PC} + t_{mux} + \max(t_{ALU} + t_{mux}, t_{mem}) + t_{setup} \\&= t_{pcq_PC} + t_{mux} + t_{mem} + t_{setup} \\&= [30 + 25 + 250 + 20] \text{ ps} \\&= \mathbf{325 \text{ ps}}\end{aligned}$$

In this example a Synchronous memory is considered.

Multicycle Performance Example

Program with 100 billion instructions

$$\begin{aligned}\text{Execution Time} &= (\# \text{ instructions}) \times \text{CPI} \times T_c \\ &= (100 \times 10^9)(4.12)(325 \times 10^{-12}) \\ &= \mathbf{133.9 \text{ seconds}}\end{aligned}$$